
Why grid

IR analysis starts from a resistive grid and sink current

The idea


- GOLDEN: 4 nodes, 3 series edges

Series path

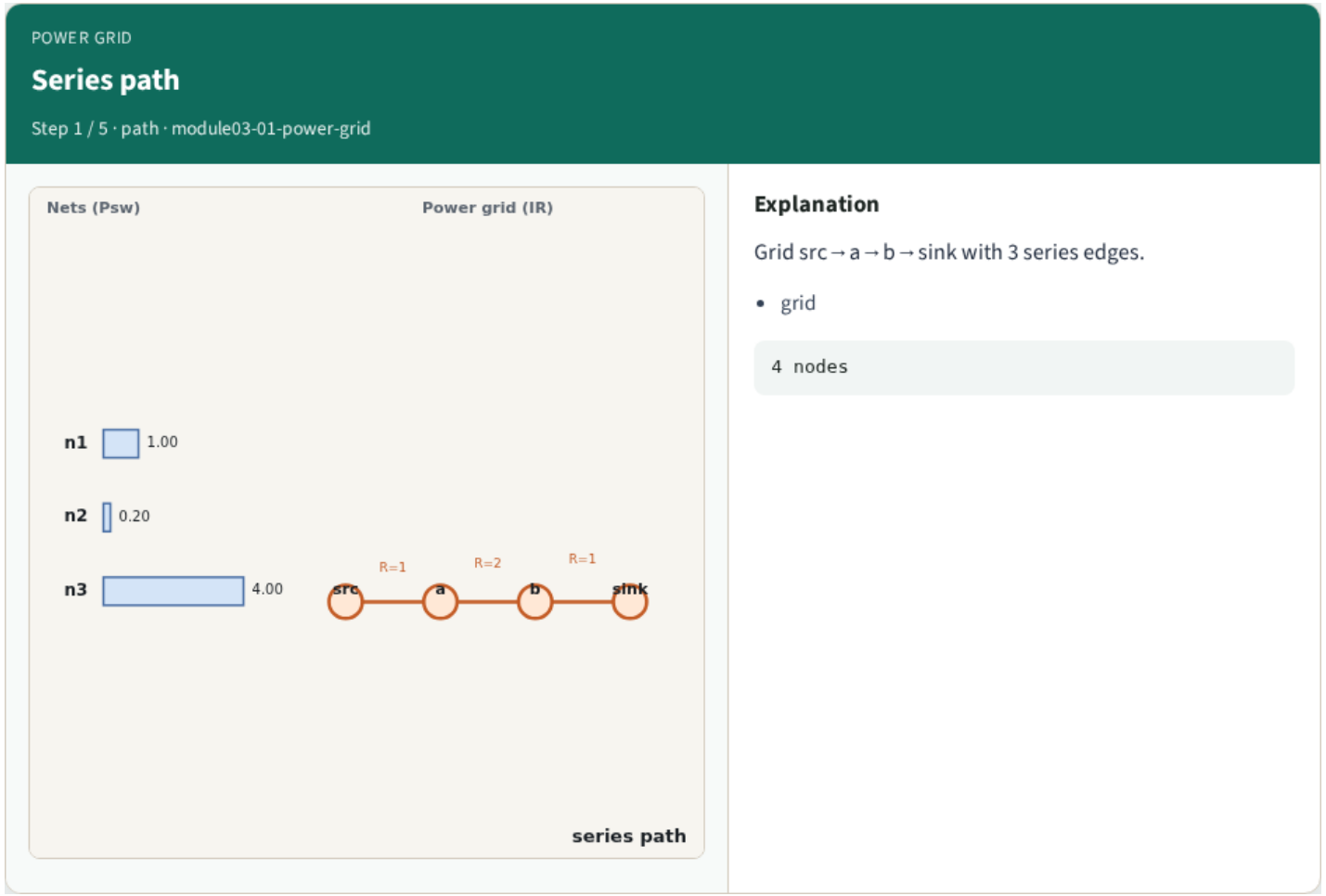


Series path

Edge e1

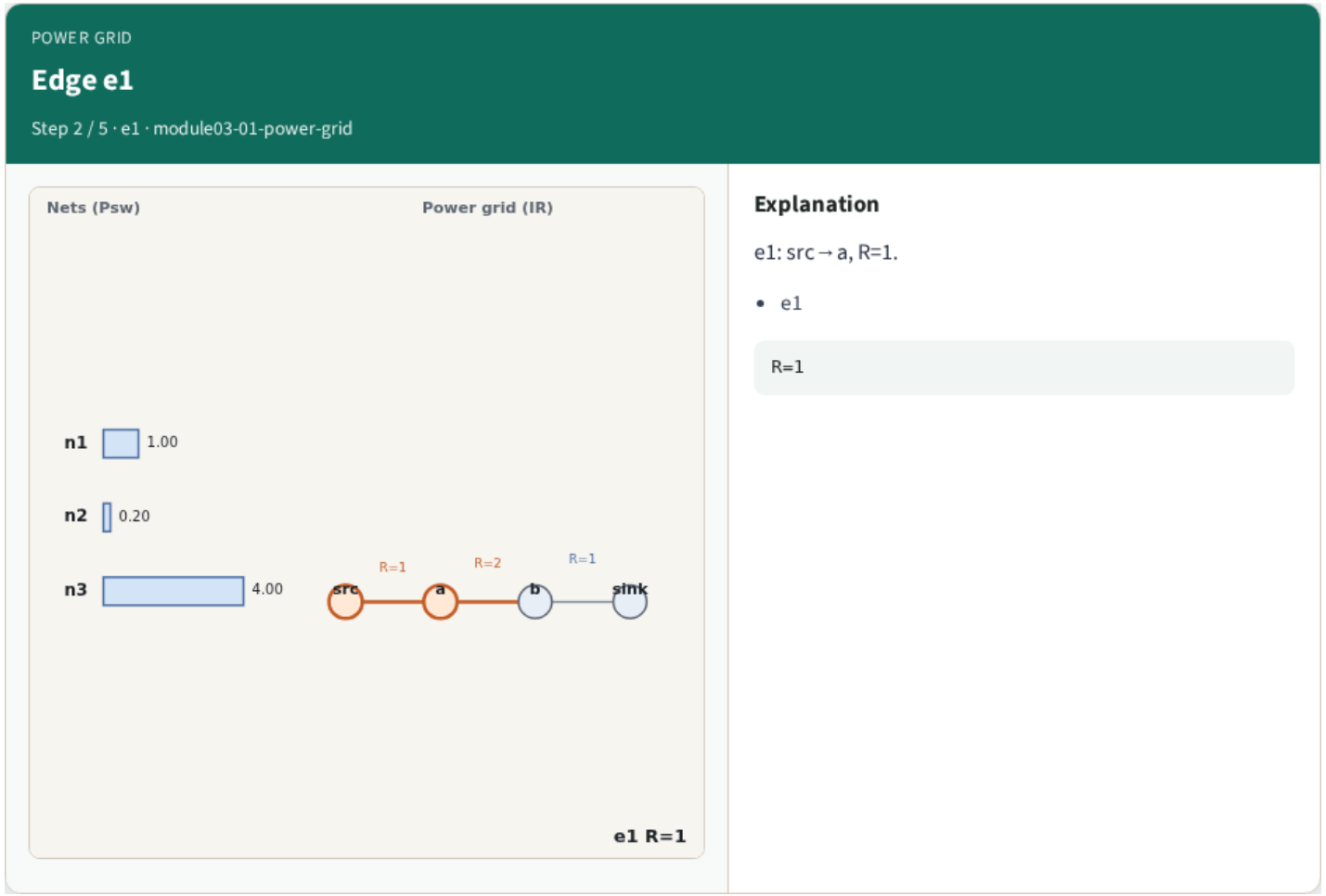


Edge e1

Edge e2

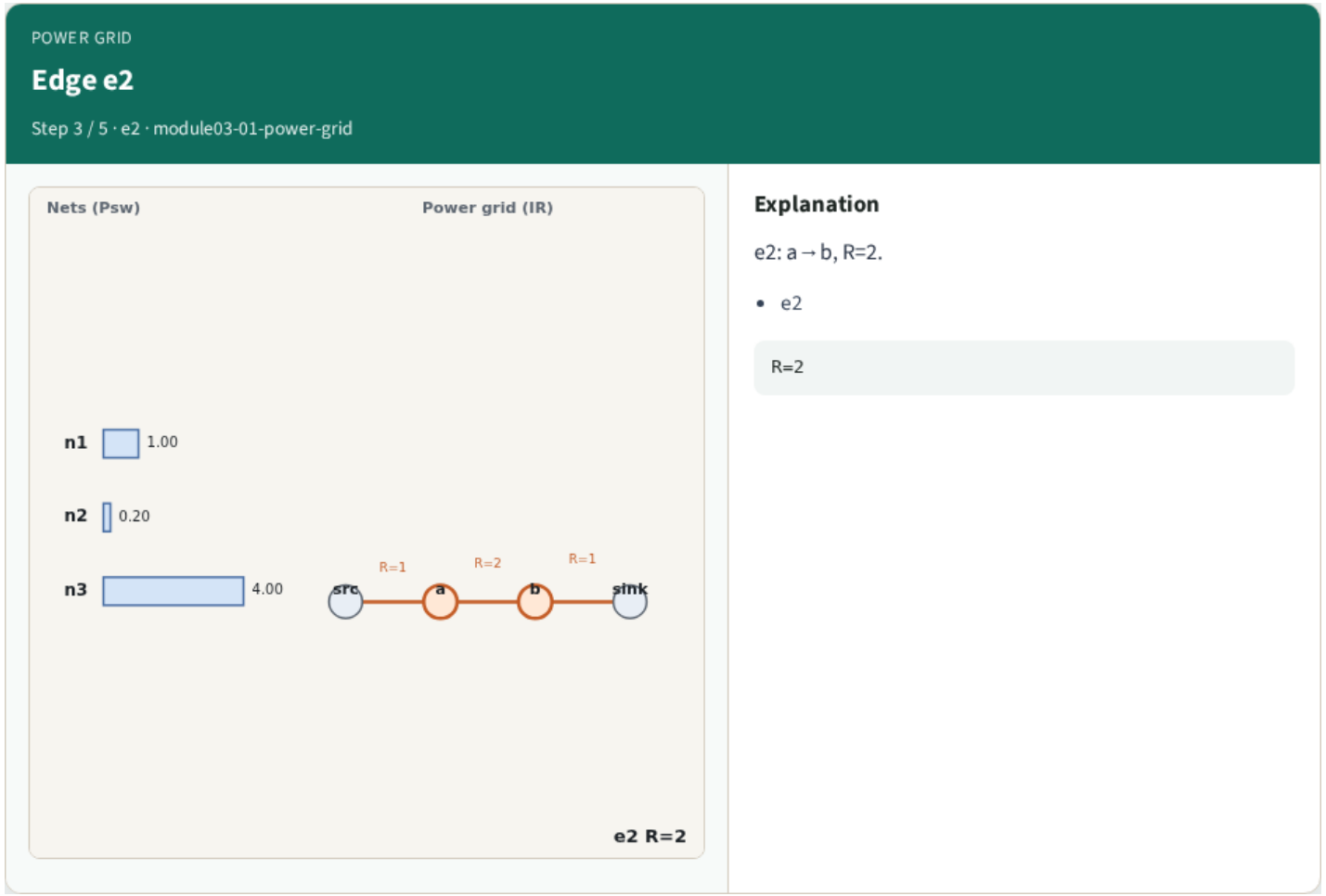

Edge e2

Edge e3

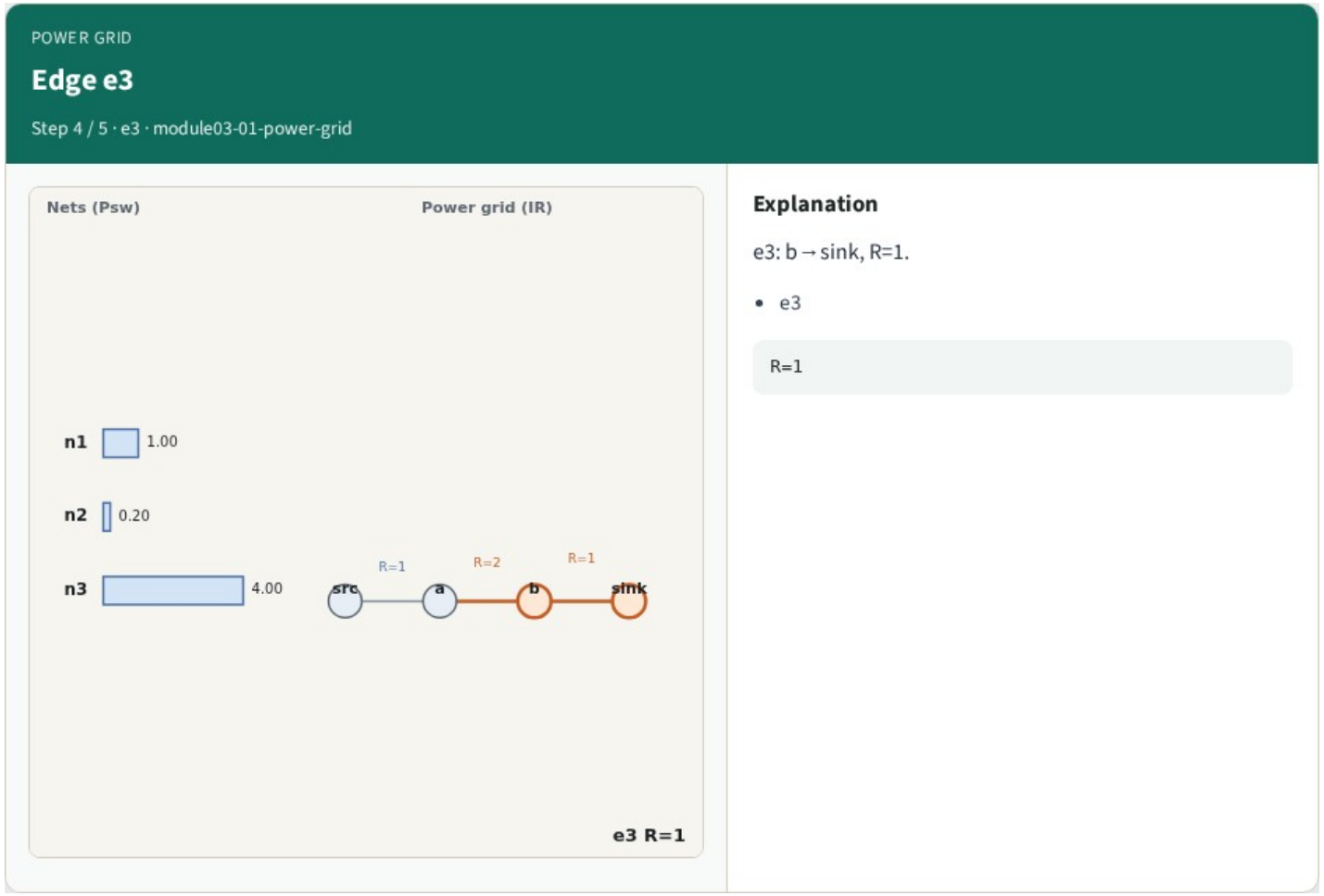


Edge e3

Golden

POWER GRID

Golden

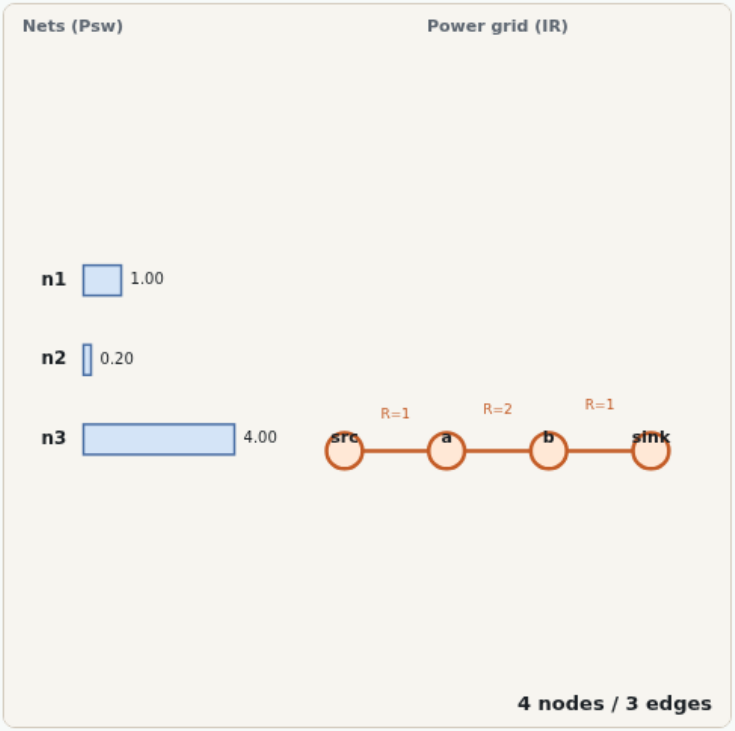Step 5 / 5 · golden · module03-01-power-grid



Explanation


GOLDEN: 4 nodes, 3 edges series.

- GOLDEN

```
4/3
```

Golden

Browser lab track

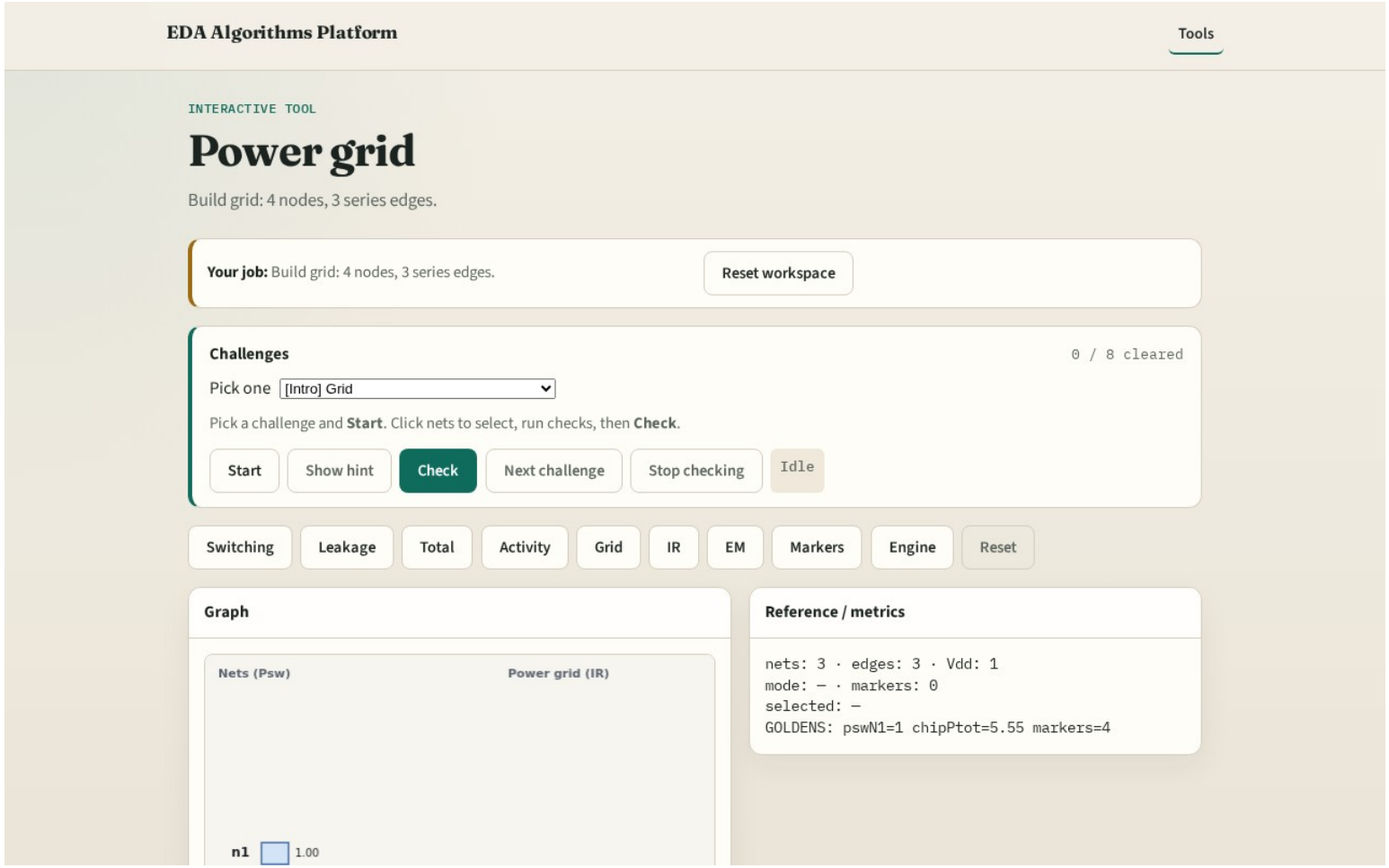

Browser lab starter

Implement track

- Call build_power_grid(); assert edge_count==3

Pitfalls

- Treating grid as parallel
- Wrong node order

Your turn

- Next: IR drop