
Why IR drop

Same sink current on every edge; accumulate I·R drops

The idea

- GOLDEN: ir_drop_sink=0.4, v_sink=0.6

IR solve

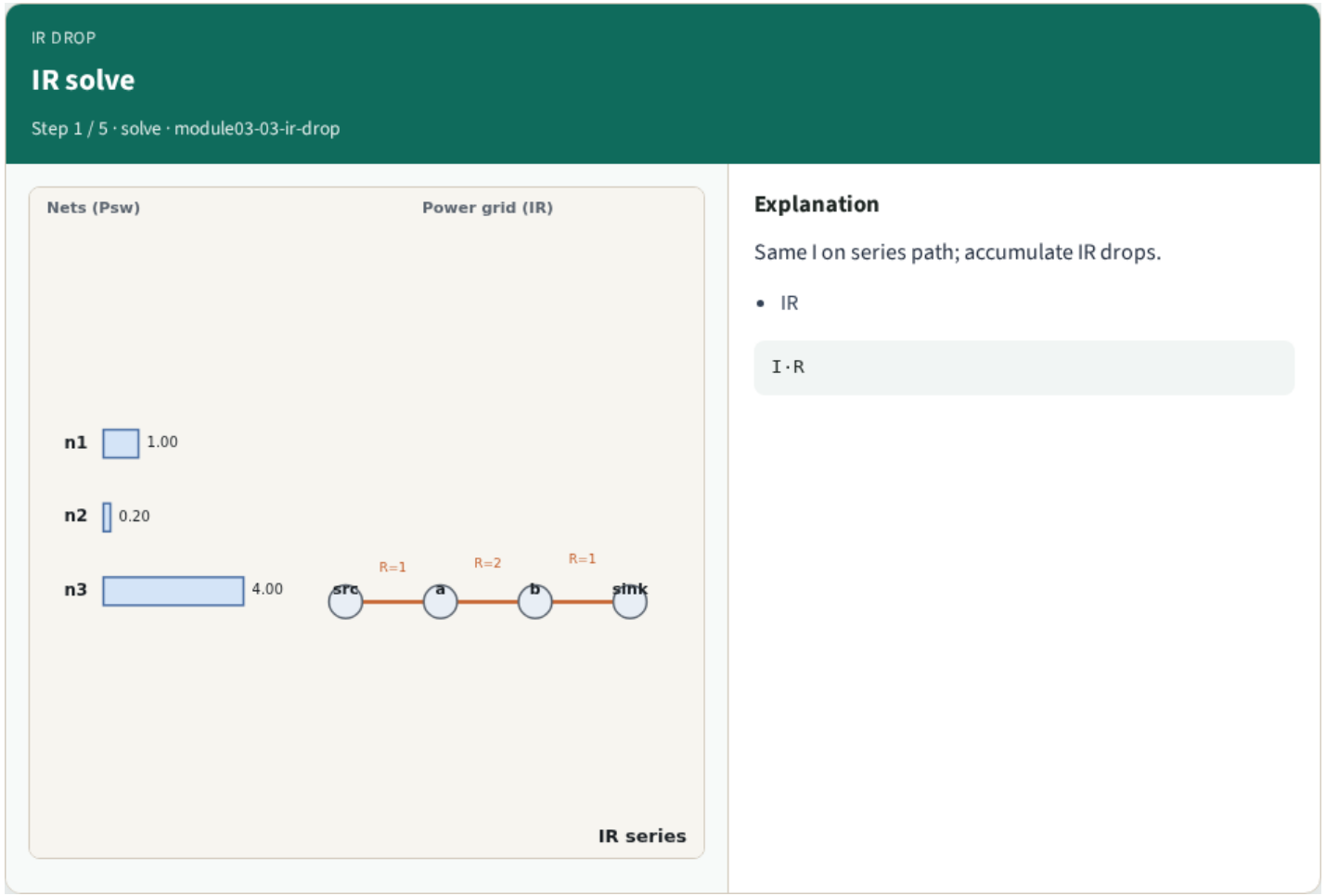


IR solve

Current

IR DROP

Current

Step 2 / 5 · i · module03-03-ir-drop

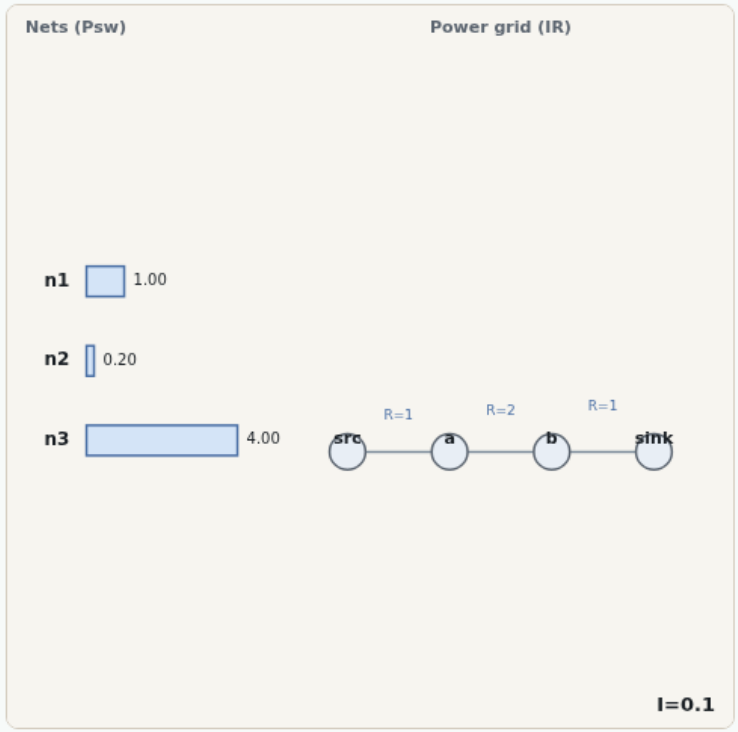

Explanation

i_sink=0.1 A on every edge.

- i_sink

```
0.1
```


Current

Edge drops

IR DROP

Edge drops

Step 3 / 5 · drops · module03-03-ir-drop

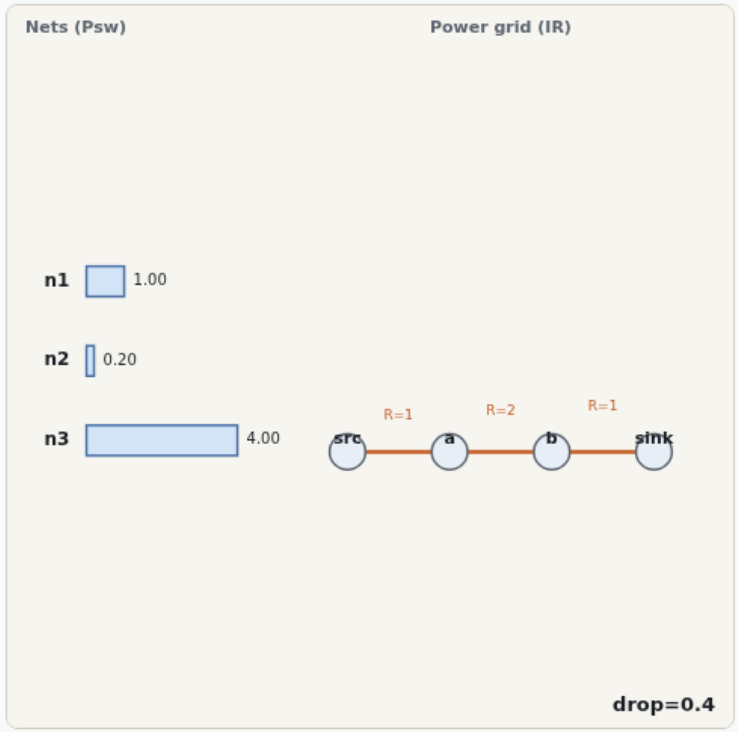

Explanation


Drops 0.1 + 0.2 + 0.1 = 0.4 V.

- drops

```
0.4
```


Edge drops

Sink voltage

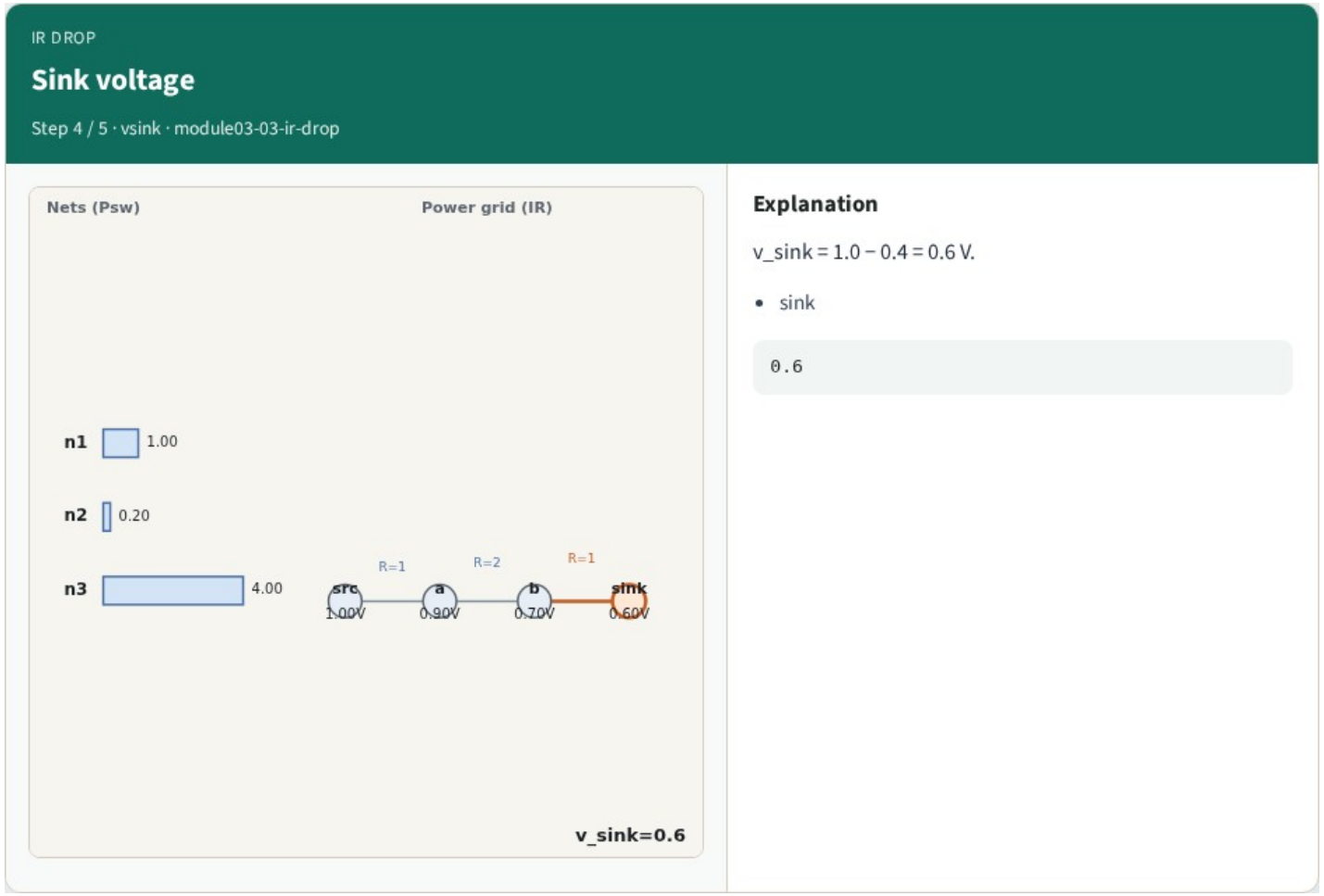


Sink voltage

Golden

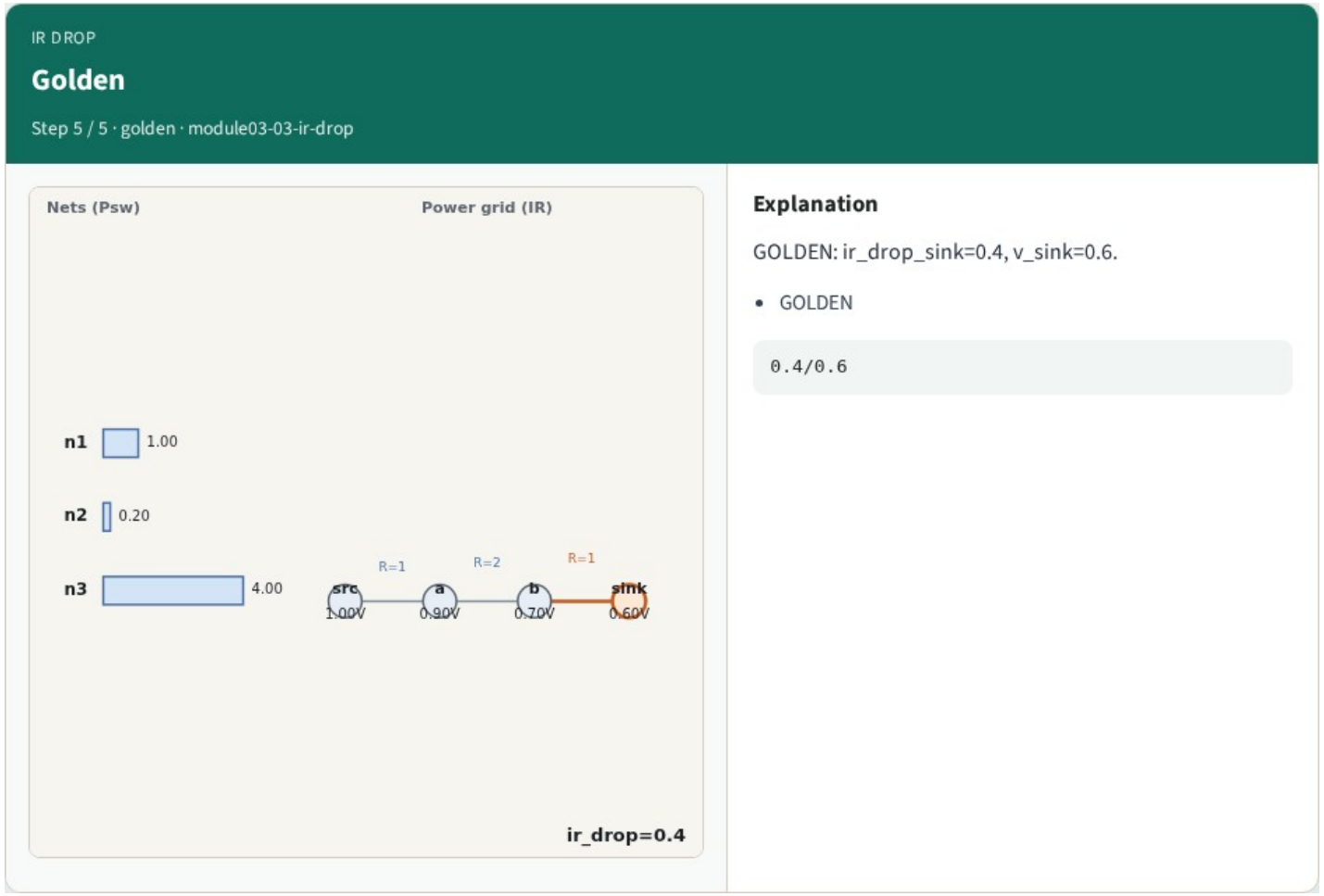

Golden

Browser lab track

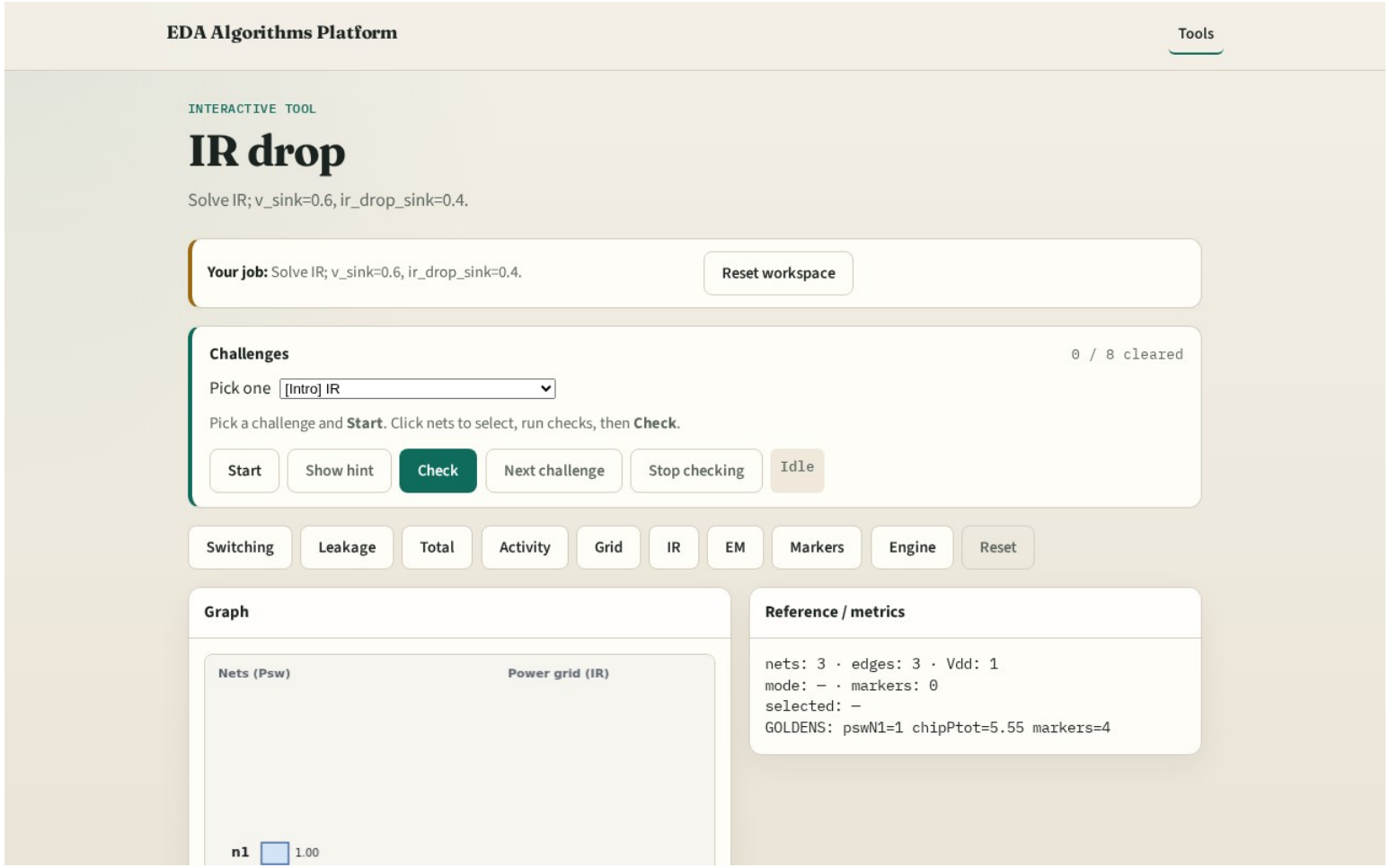

Browser lab starter

Implement track

- Call ir_drop_solve(); assert v_sink==0.6 and ir_drop_sink==0.4

Pitfalls

- Using parallel formula
- Wrong edge order

Your turn

- Next: EM literacy