
Why area map

Techmap maps AND/NOR to a NAND2 library minimizing cell count

The idea


- GOLDEN: techmap_nand_count_area=6

NAND2 library

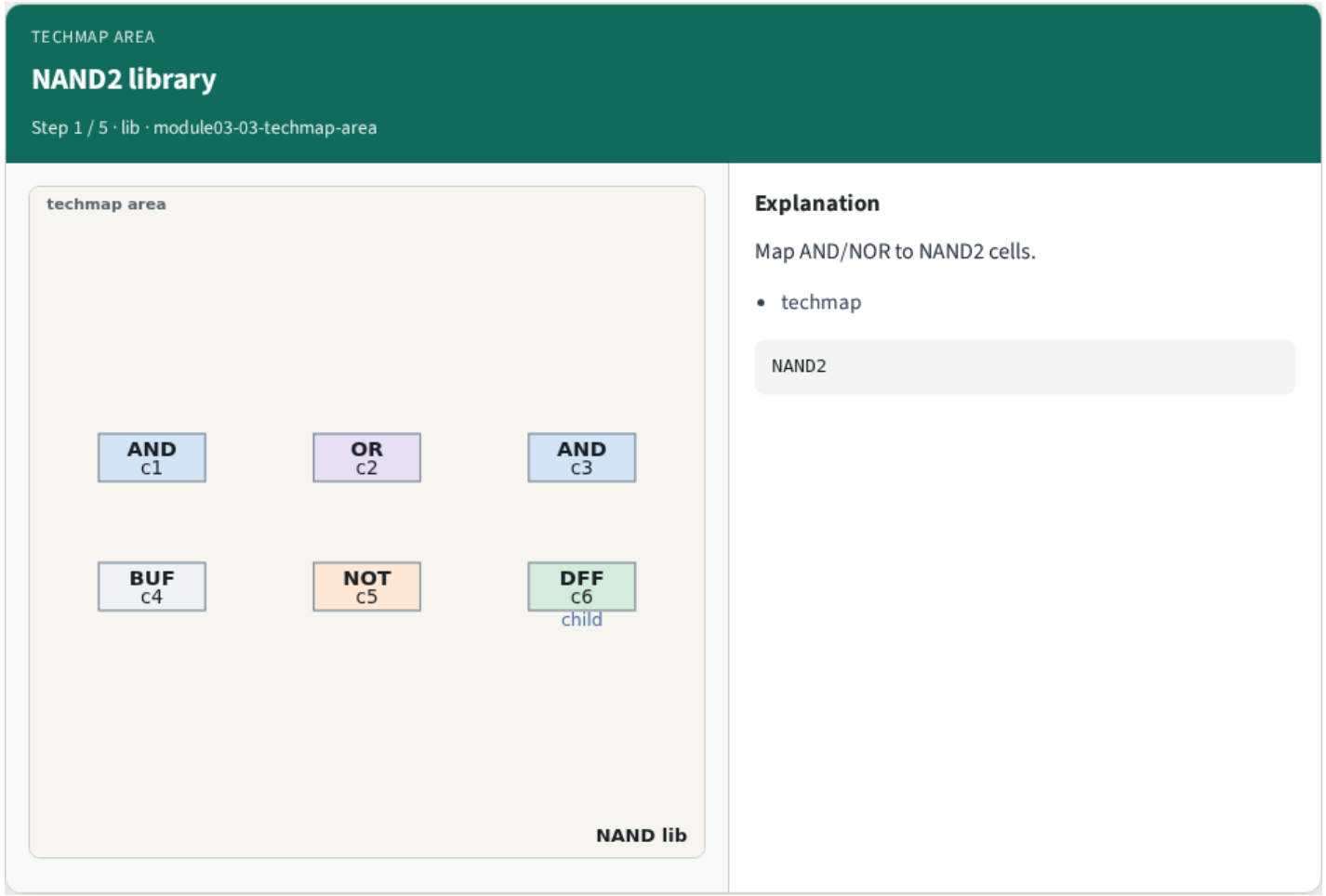


NAND2 library

AND → 2 NAND

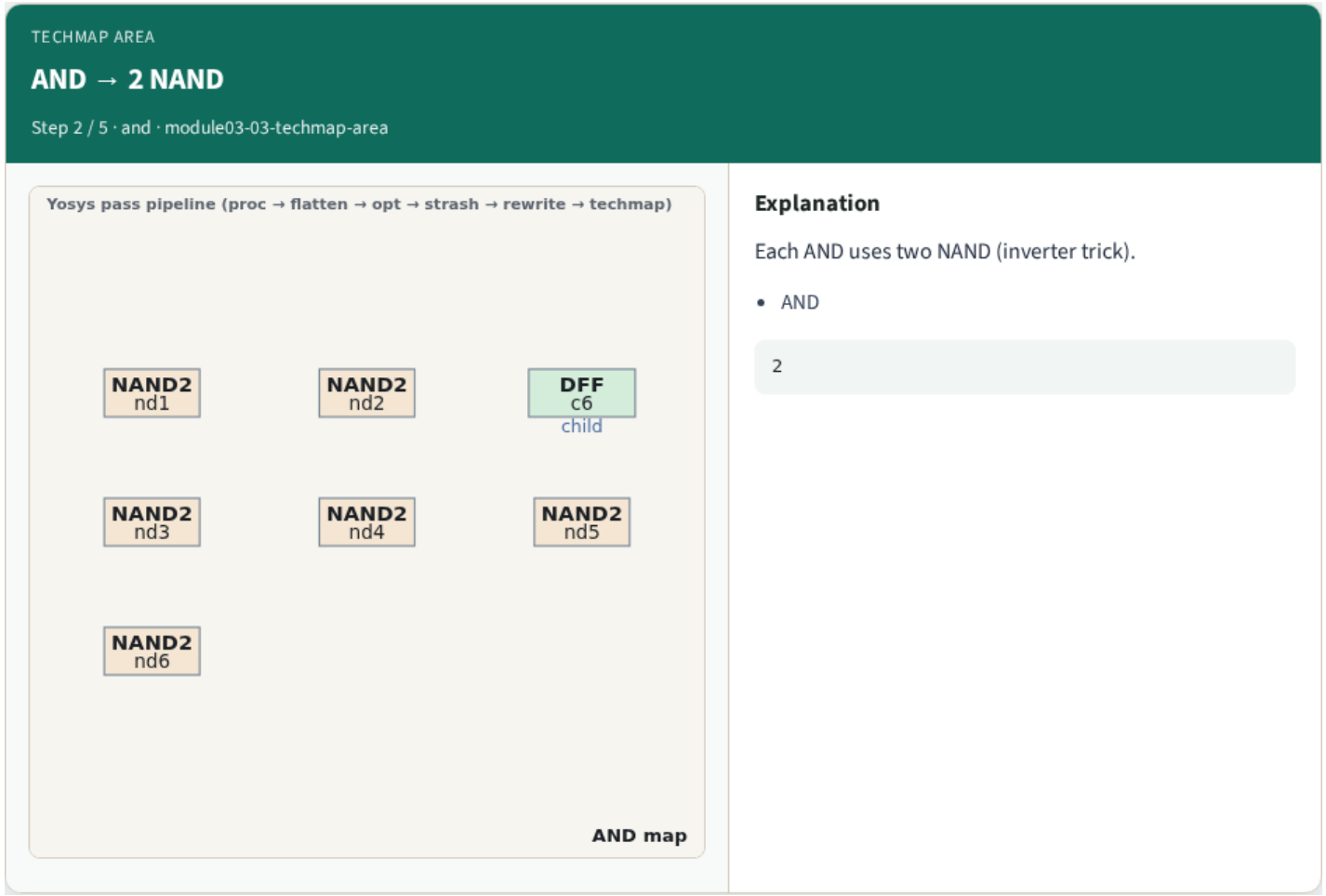


AND → 2 NAND

NOR → 4 NAND

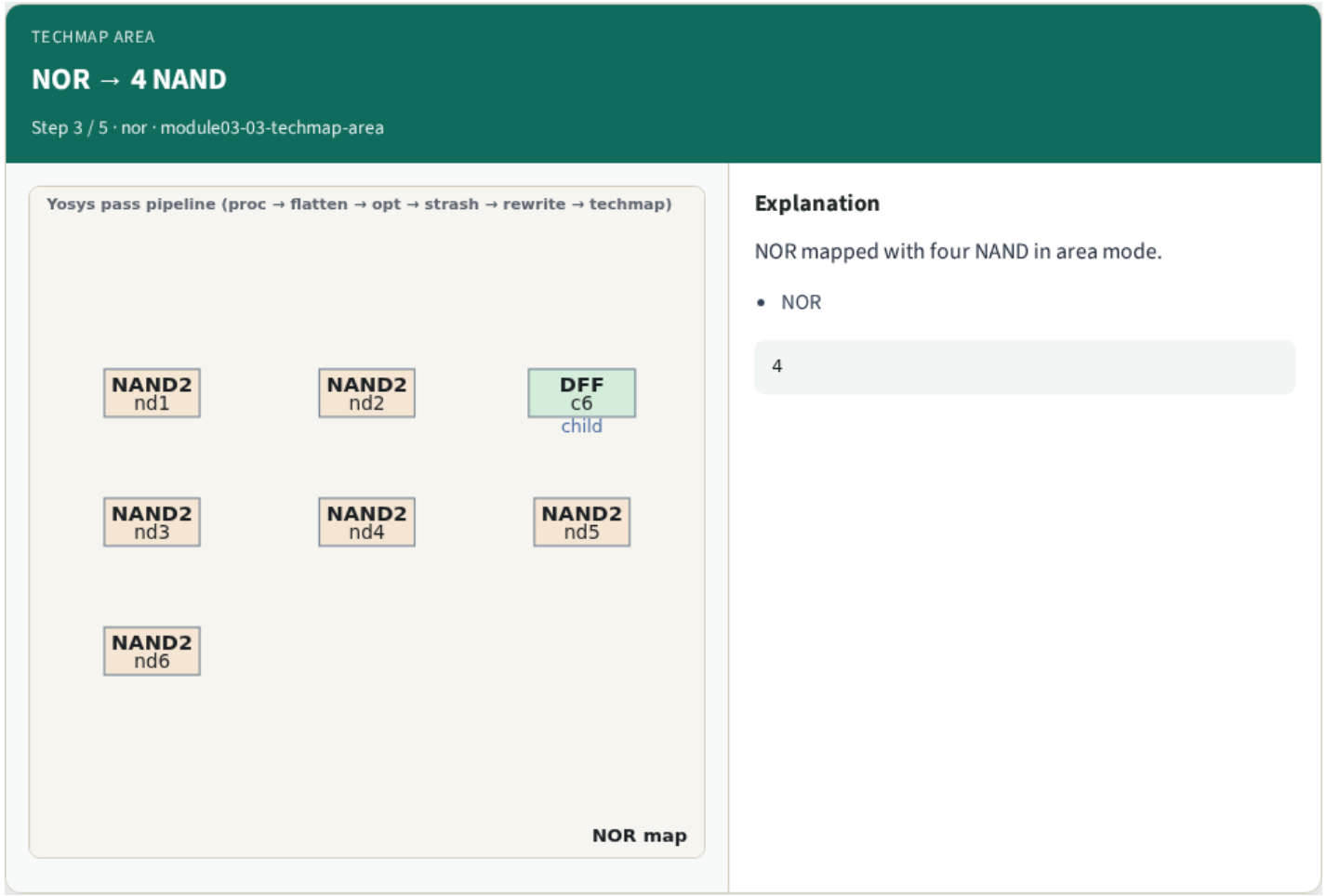


NOR → 4 NAND

NAND count

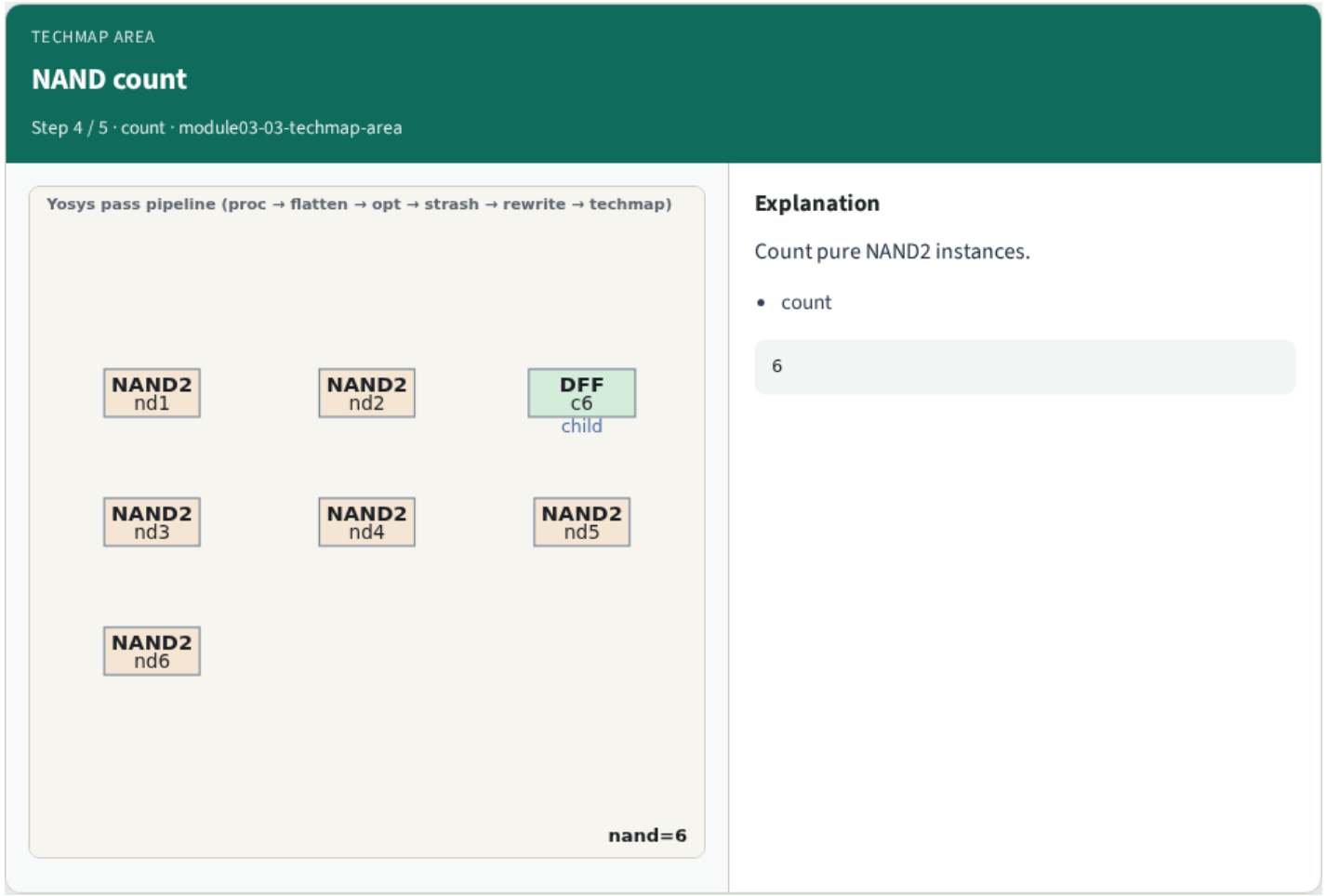


NAND count

Golden

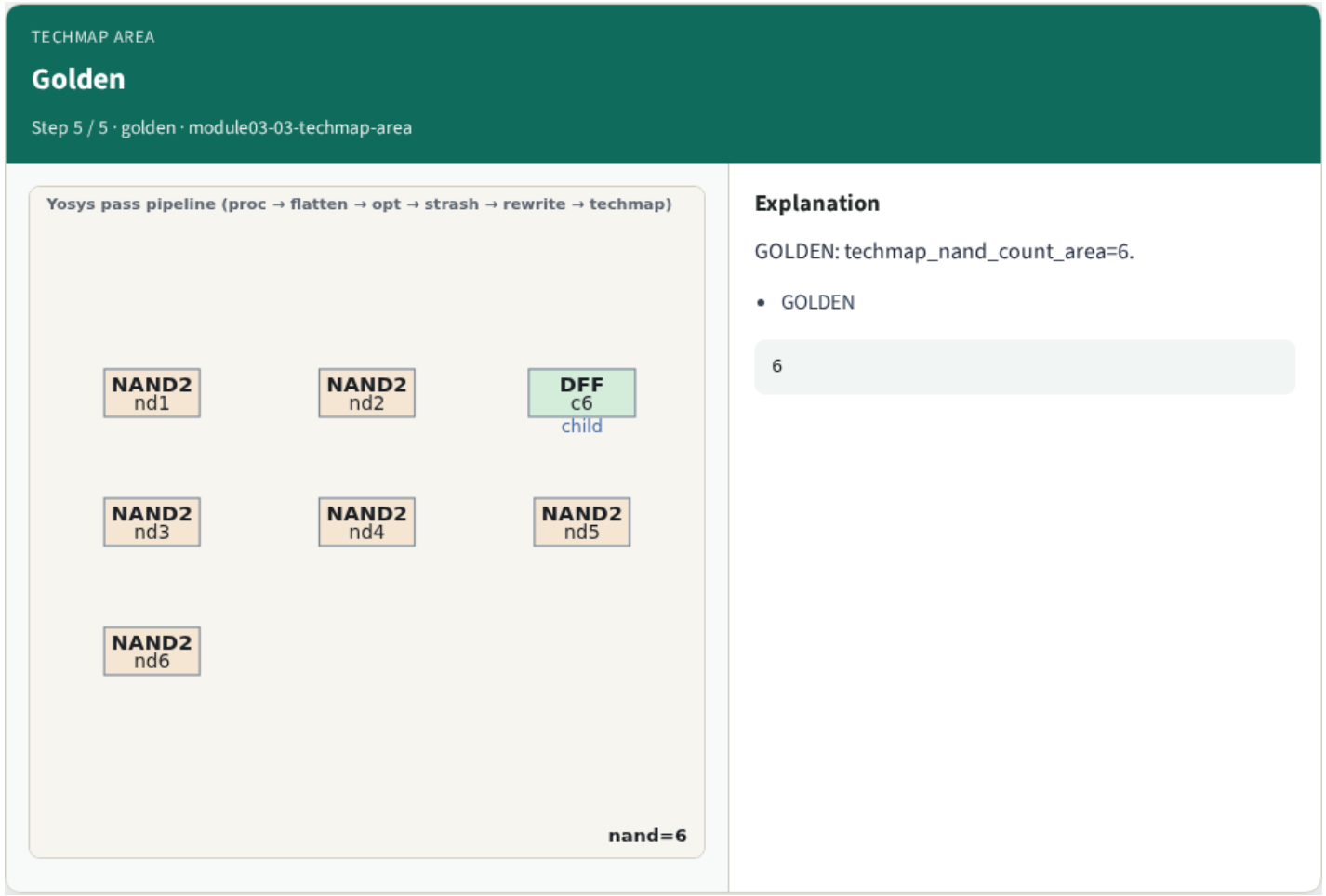

Golden

Browser lab track

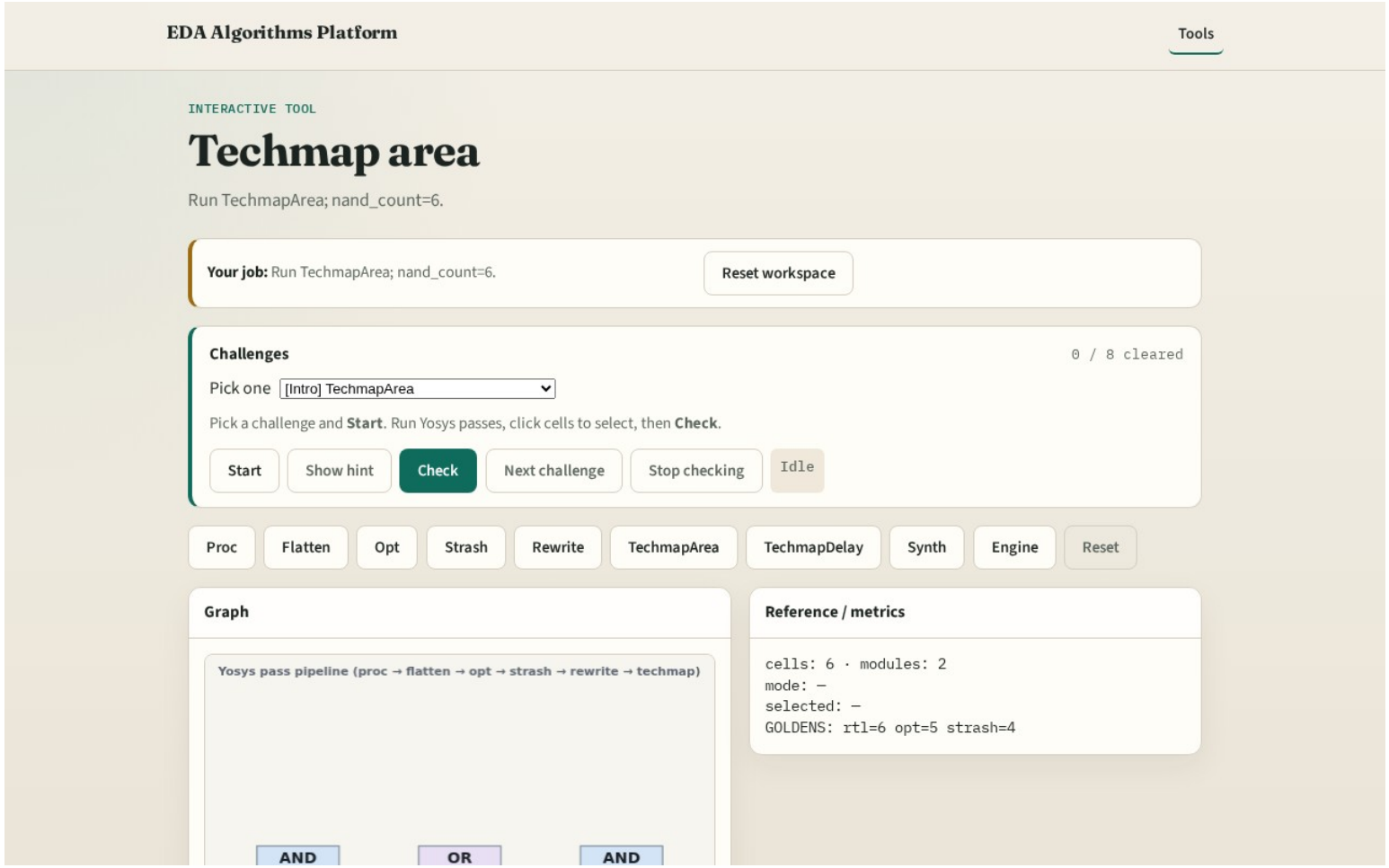

Browser lab starter

Implement track

- Call pass_techmap(mode='area'); assert nand_count==6

Pitfalls

- Counting DFF as NAND
- Using delay mapping

Your turn

- Next: techmap delay