
Layout graph

Layout graph mirrors schematic , devices X0/X1 with pin-to-net edges

The idea


- GOLDEN: 2 devices, 4 nets, 6 edges

Devices

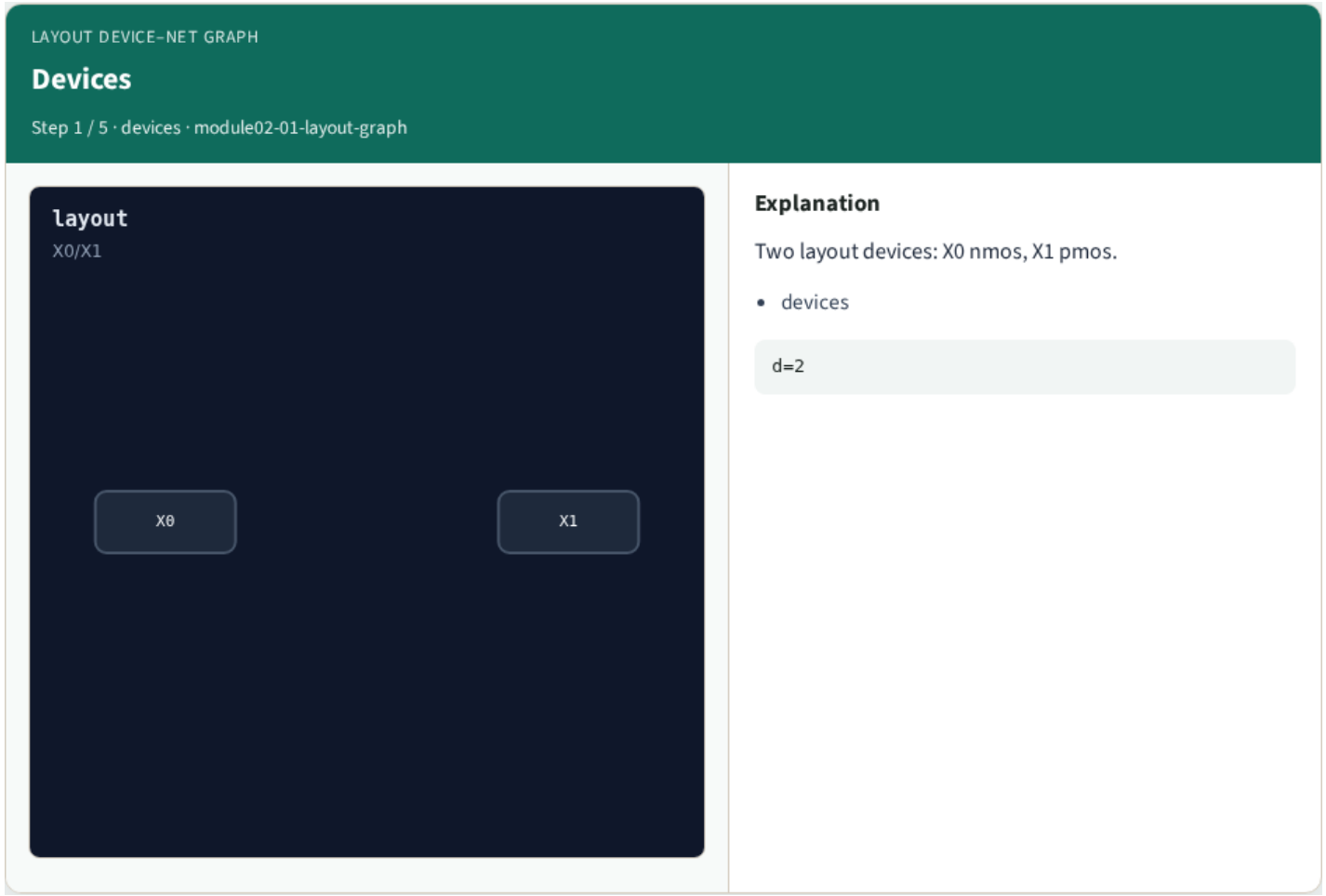


Devices

Nets

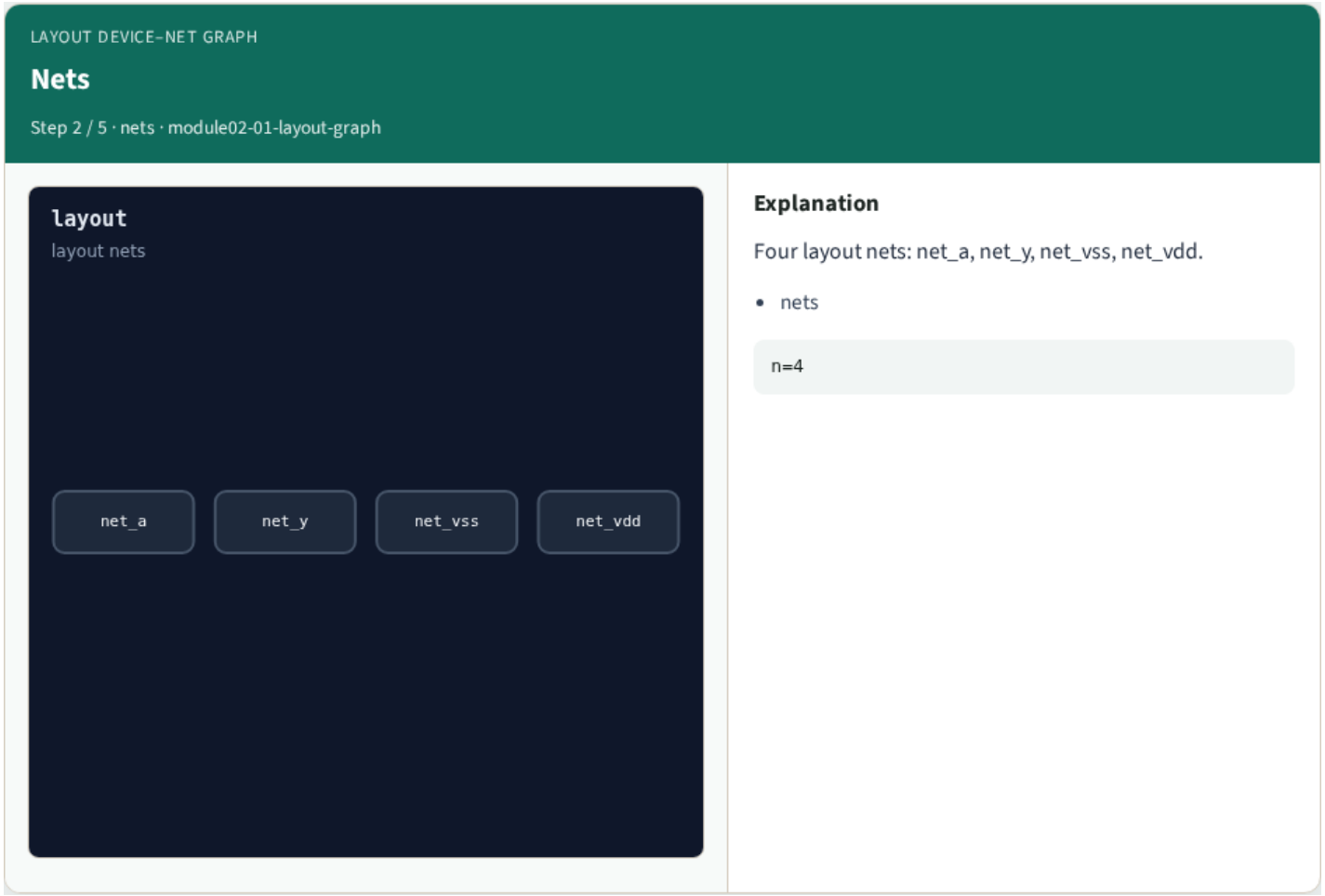
LAYOUT DEVICE–NET GRAPH
Nets
Step 2 / 5 · nets · module02-01-layout-graph
layout
layout nets
net_a
net_y
net_vss
net_vdd
Explanation
Four layout nets: net_a, net_y, net_vss, net_vdd.
nets
n=4


Nets

Pins

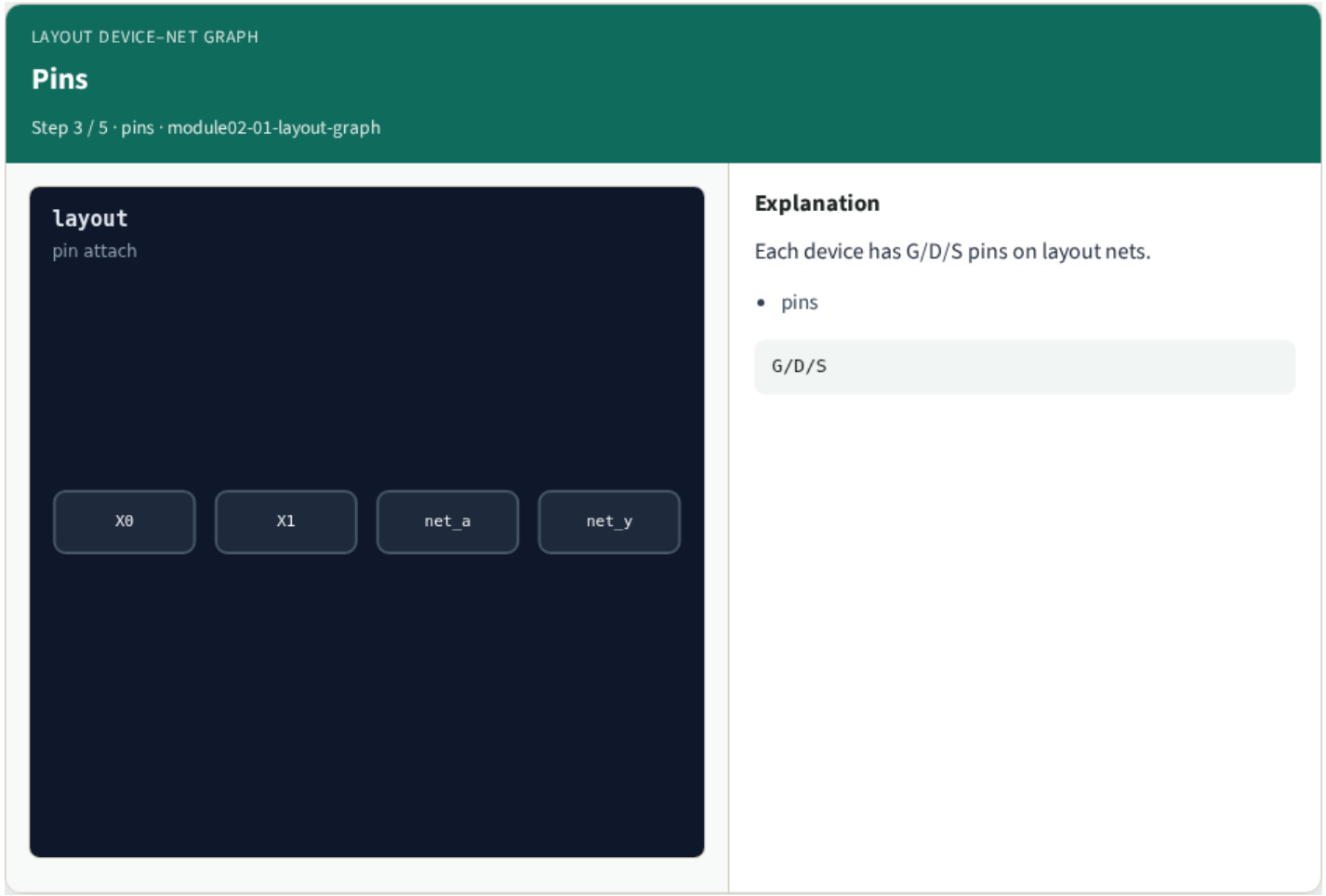
LAYOUT DEVICE–NET GRAPH
Pins
Step 3 / 5 · pins · module02-01-layout-graph
layout
pin attach
X0
X1
net_a
net_y
Explanation
Each device has G/D/S pins on layout nets.
pins
G/D/S


Pins

Edges

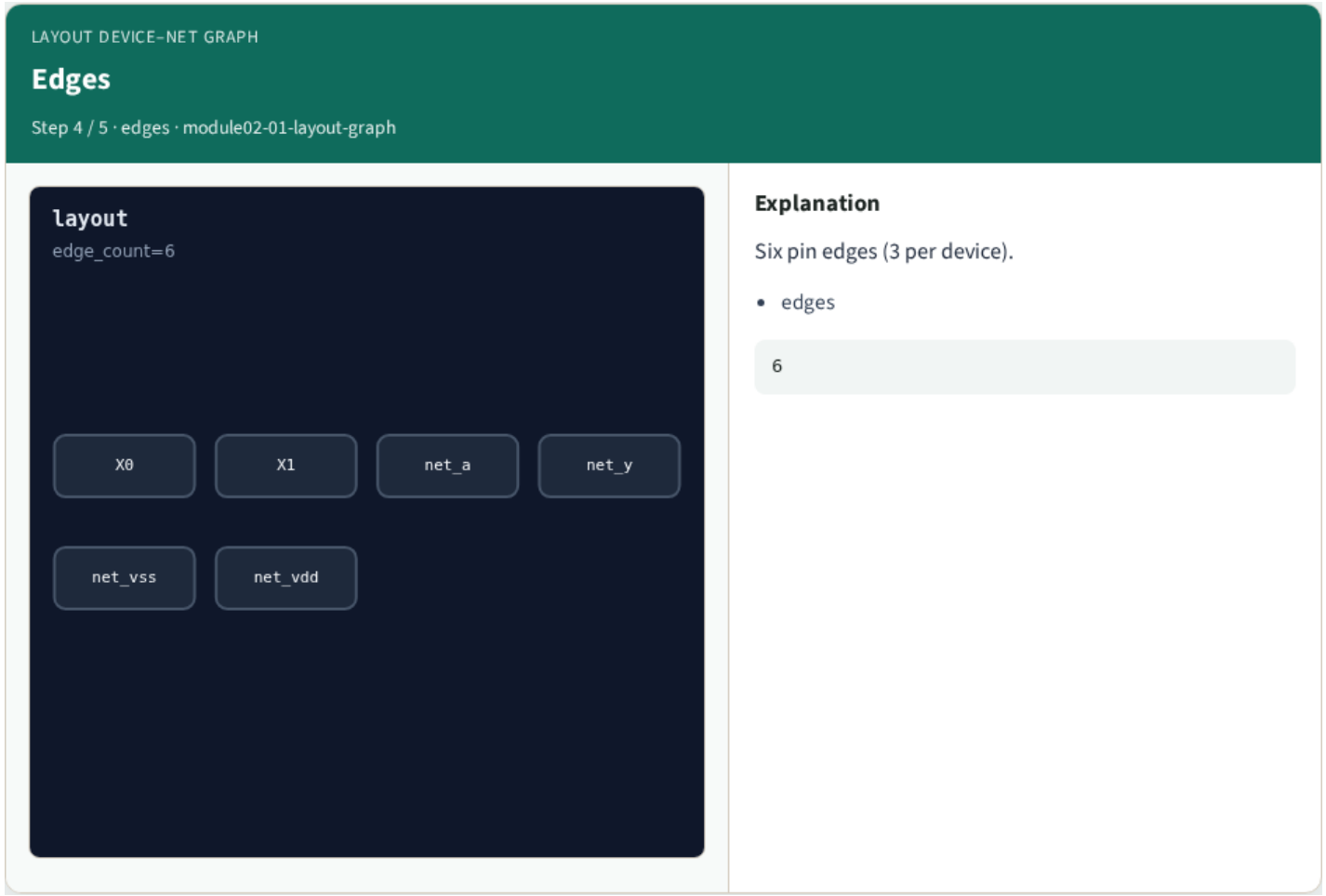
LAYOUT DEVICE-NET GRAPH
Edges
Step 4 / 5 · edges · module02-01-layout-graph
layout
edge_count=6
X0
X1
net_a
net_y
net_vss
net_vdd
Explanation
Six pin edges (3 per device).
edges
6


Edges

Golden

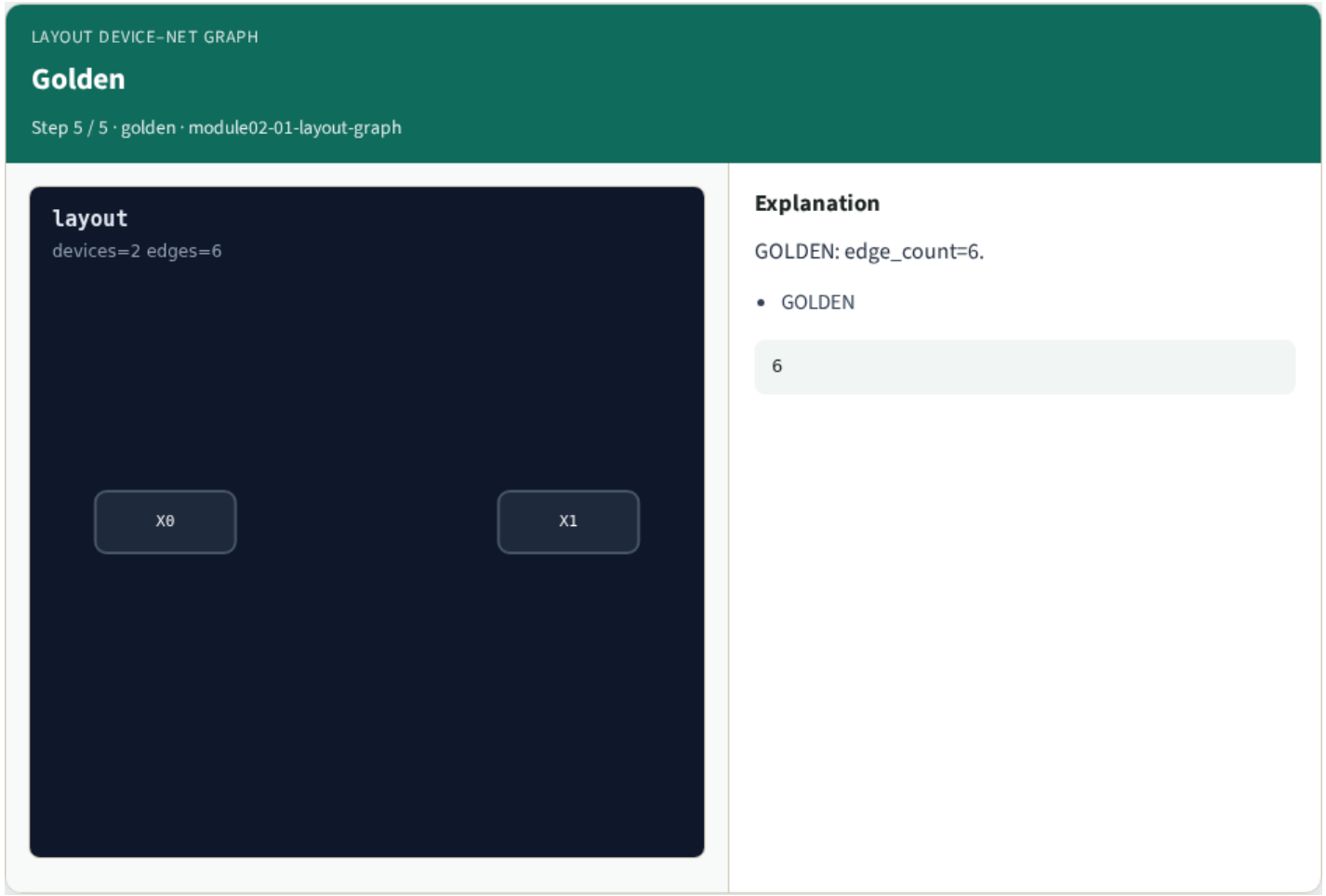

Golden

Browser lab track

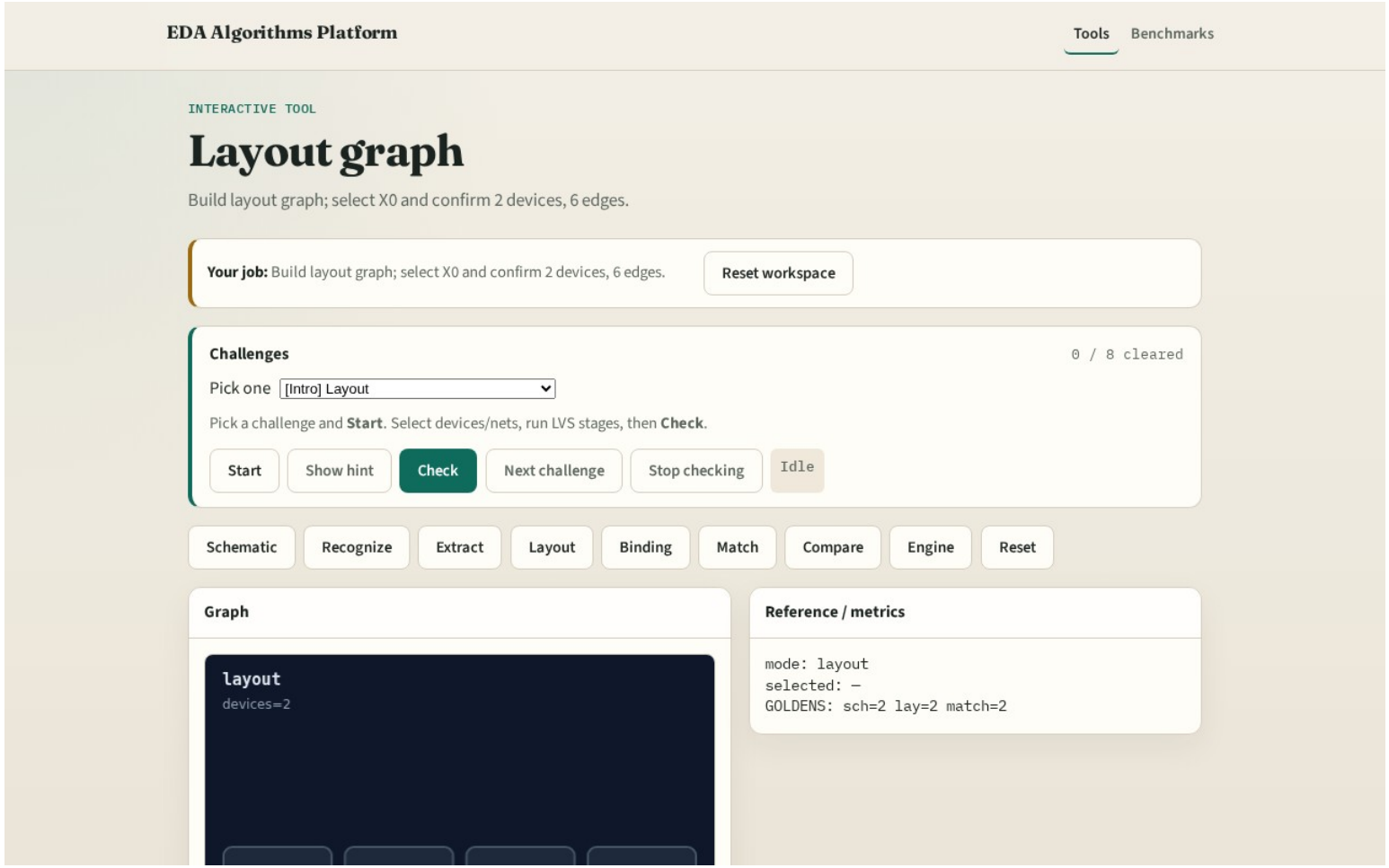

Browser lab starter

Implement track

- Call layout_graph(); assert device_count==2 and edge_count==6

Pitfalls

- Using schematic net names on layout graph
- Missing a pin edge

Your turn

- Next: pin / name binding