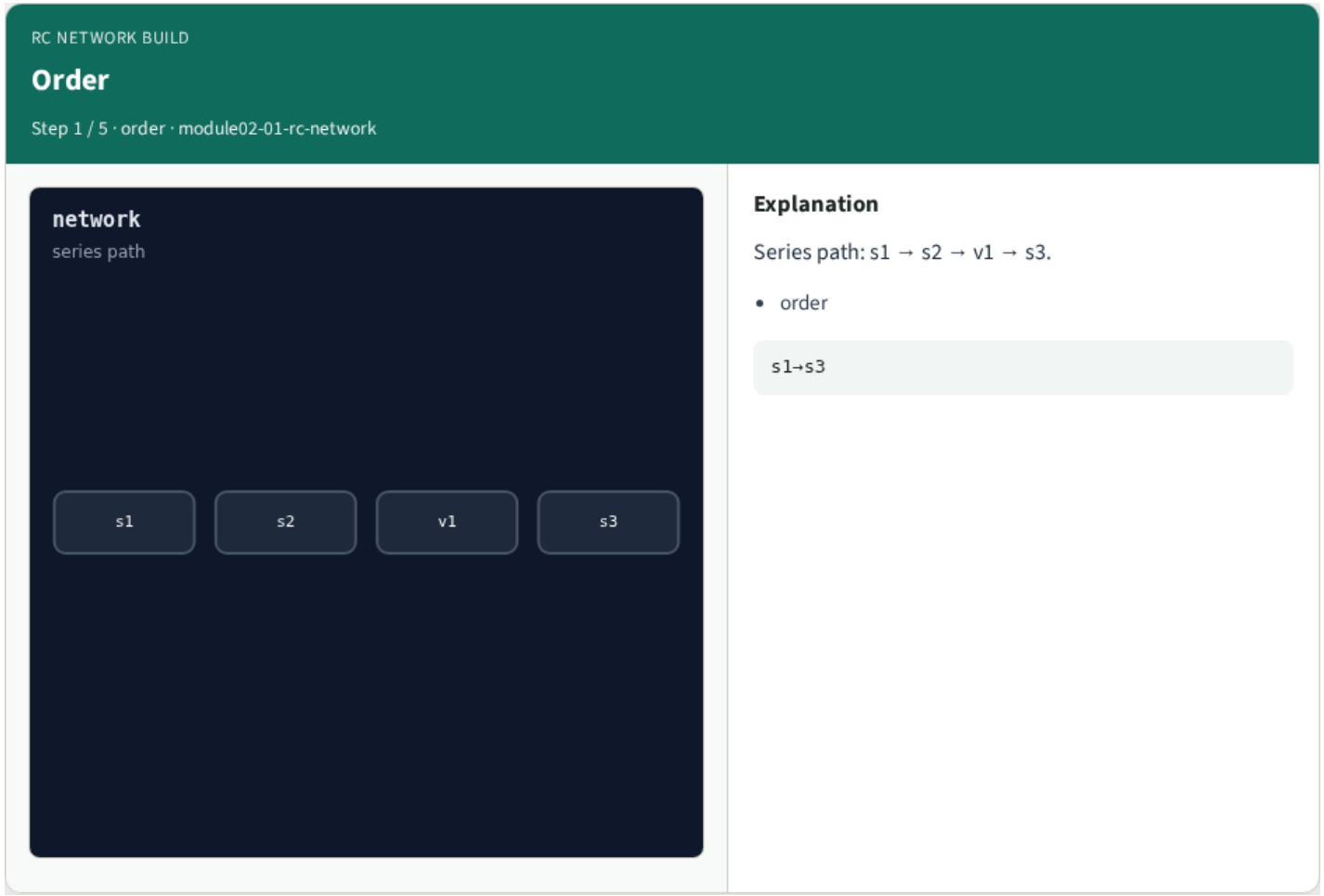
RC network

RC network chains segment resistors in series; attach ground C at metal nodes

The idea


- GOLDEN: series chain; nodes include in/out

Order


RC NETWORK BUILD
Order
Step 1 / 5 · order · module02-01-rc-network
network
series path
s1
s2
v1
s3
Explanation
Series path: s1 → s2 → v1 → s3.
order
s1→s3


Order

Resistors

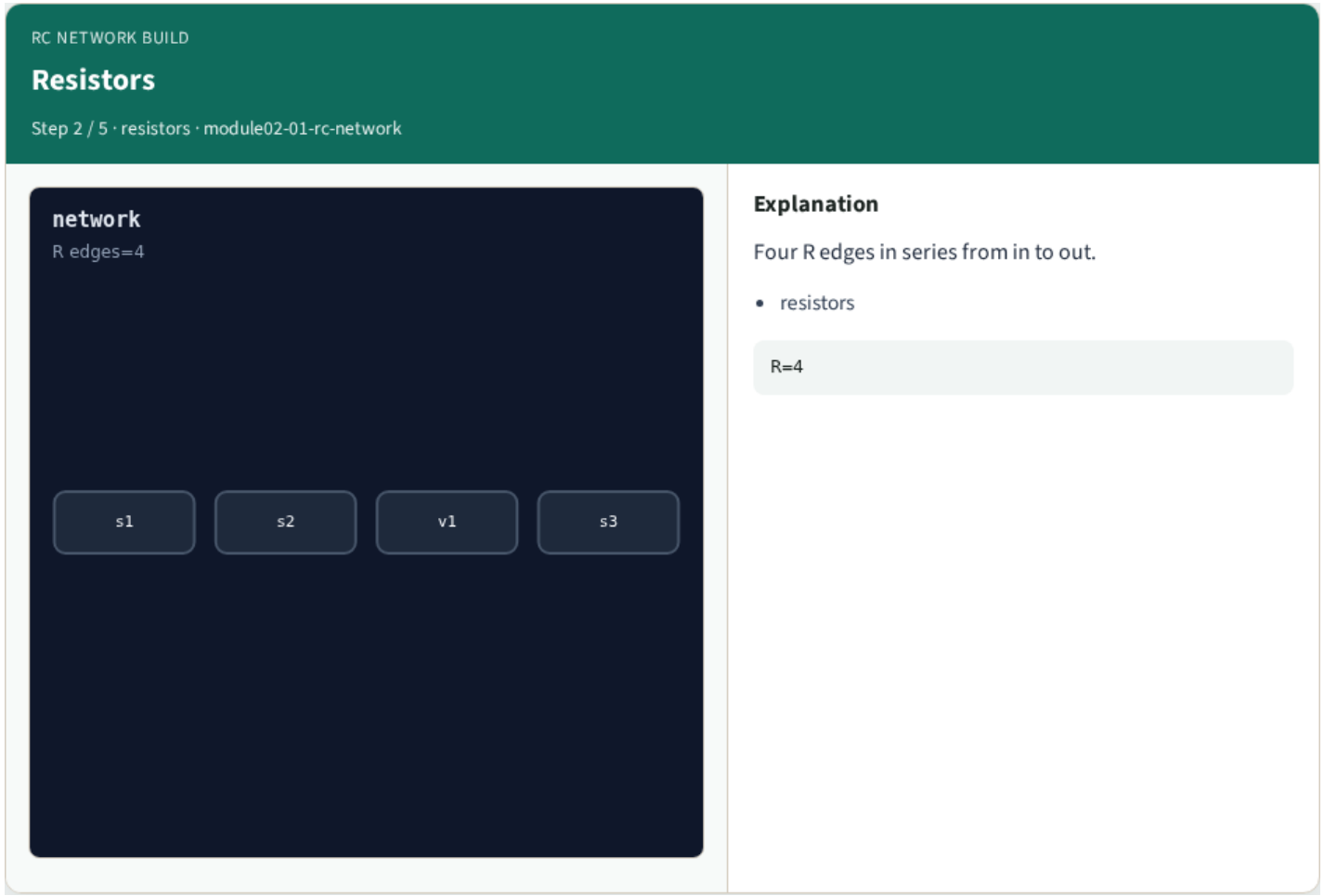


Resistors

Nodes

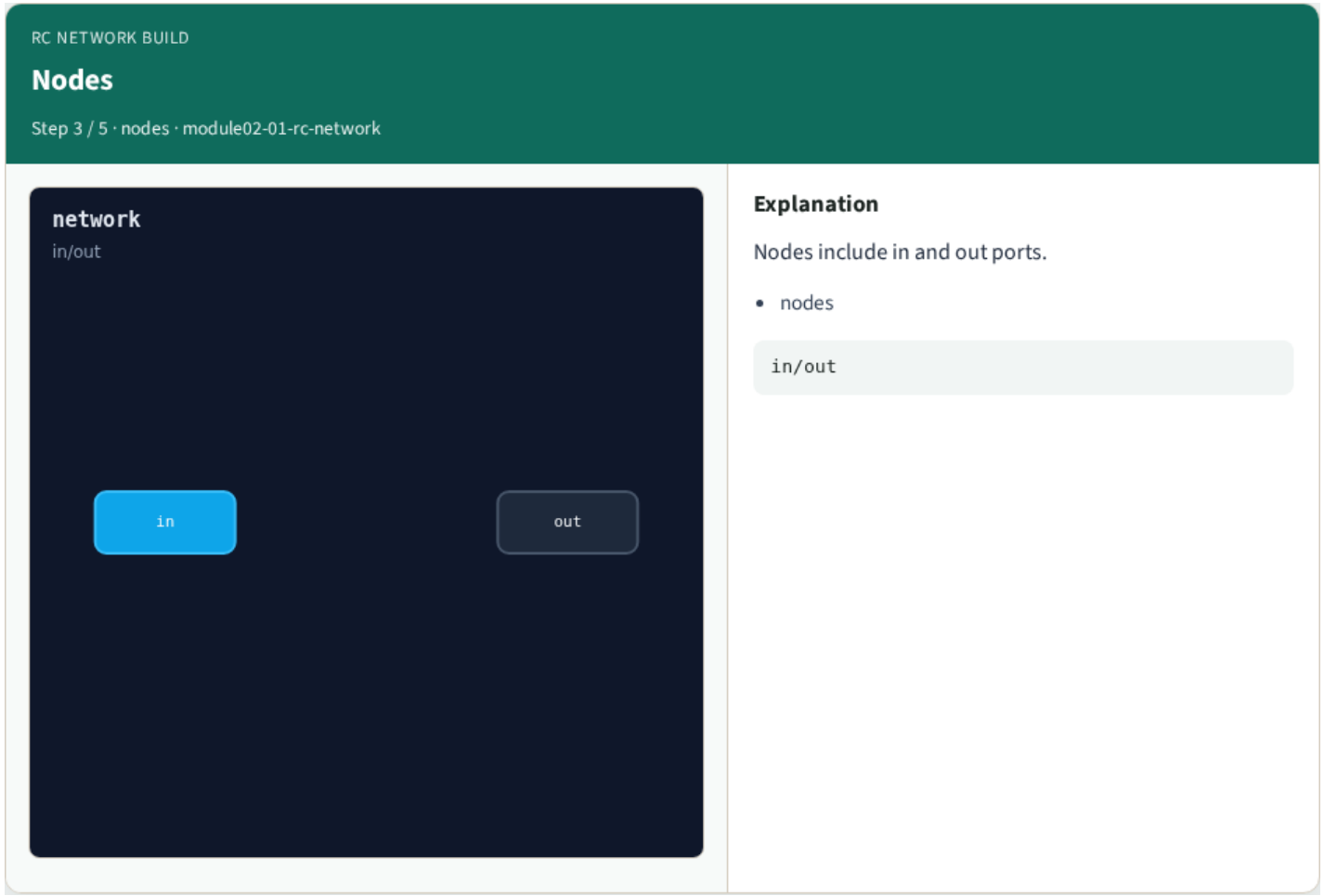
RC NETWORK BUILD
Nodes
Step 3 / 5 · nodes · module02-01-rc-network
network
in/out
in
out
Explanation
Nodes include in and out ports.
nodes
in/out


Nodes

Caps

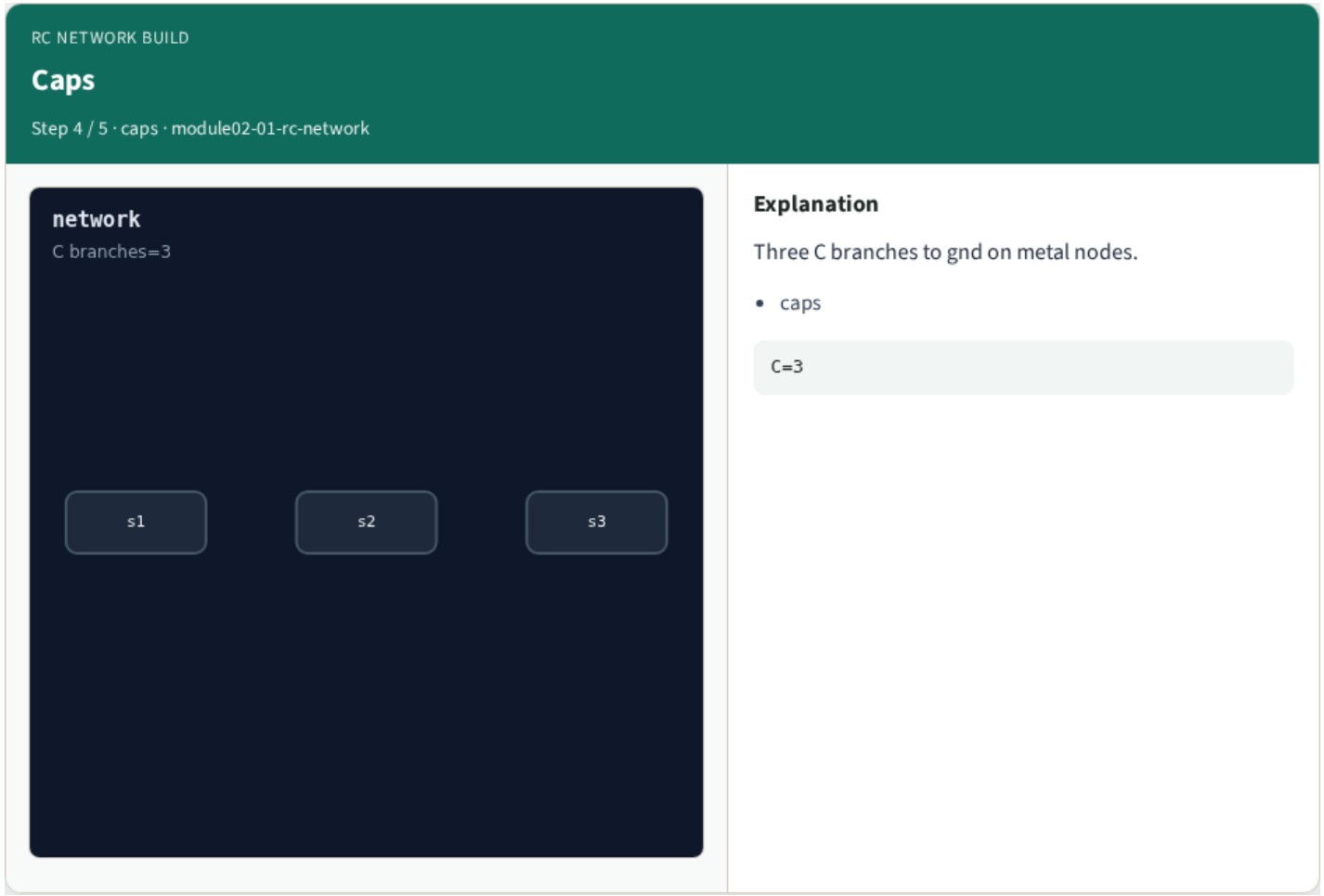
RC NETWORK BUILD
Caps
Step 4 / 5 · caps · module02-01-rc-network
network
C branches=3
s1
s2
s3
Explanation
Three C branches to gnd on metal nodes.
caps
C=3


Caps

Golden

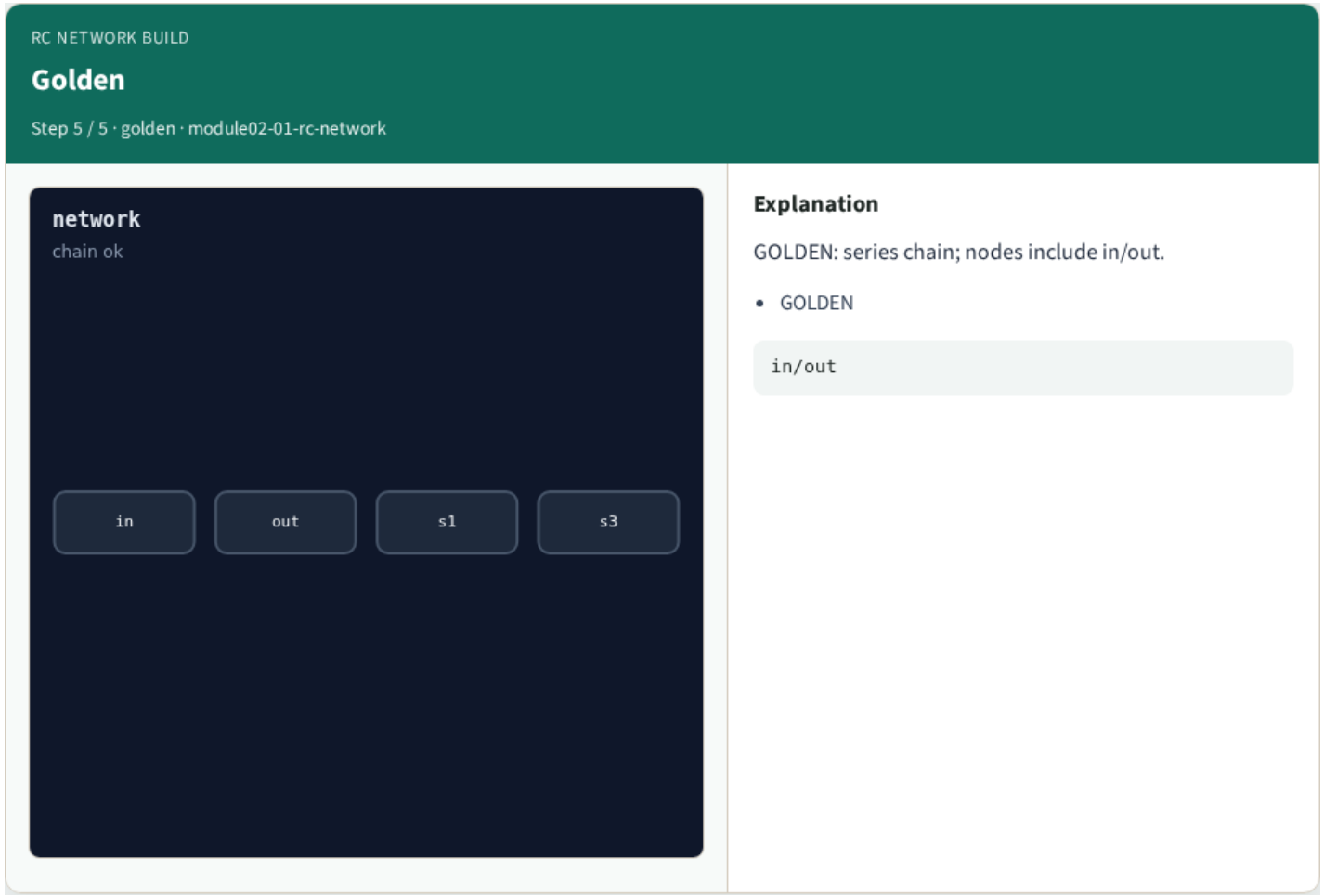

Golden

Browser lab track

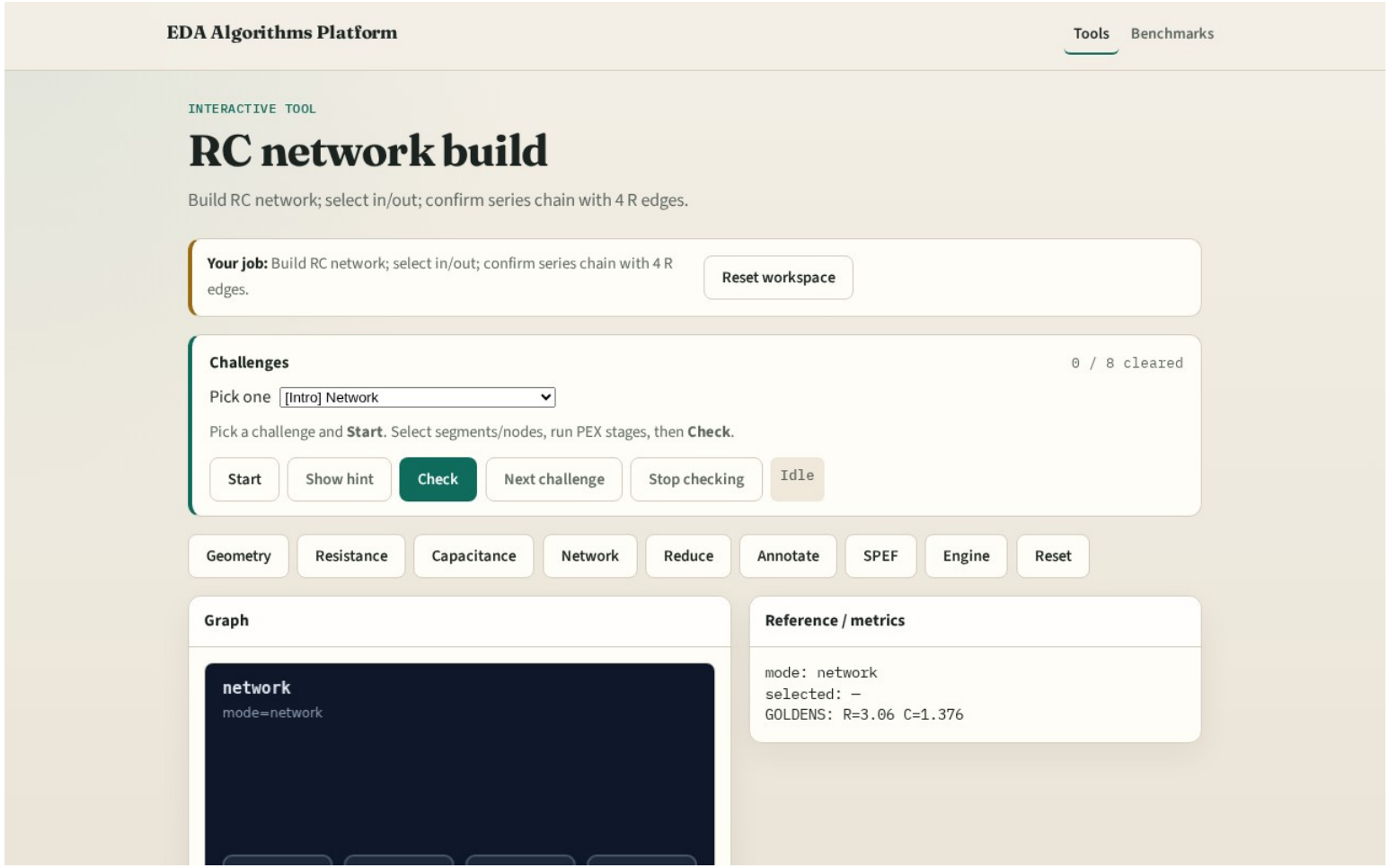

Browser lab starter

Implement track

- Call build_rc_network(); assert nodes include 'in' and 'out' and r_count==4

Pitfalls

- Parallel instead of series R
- Attaching C on VIA node

Your turn

- Next: network reduction