
Reduce

Network reduction collapses the chain to in–out R_eq and lumped C_eq

The idea


- GOLDEN: after_nodes=2; R_eq=3.06 C_eq=1.376

Before

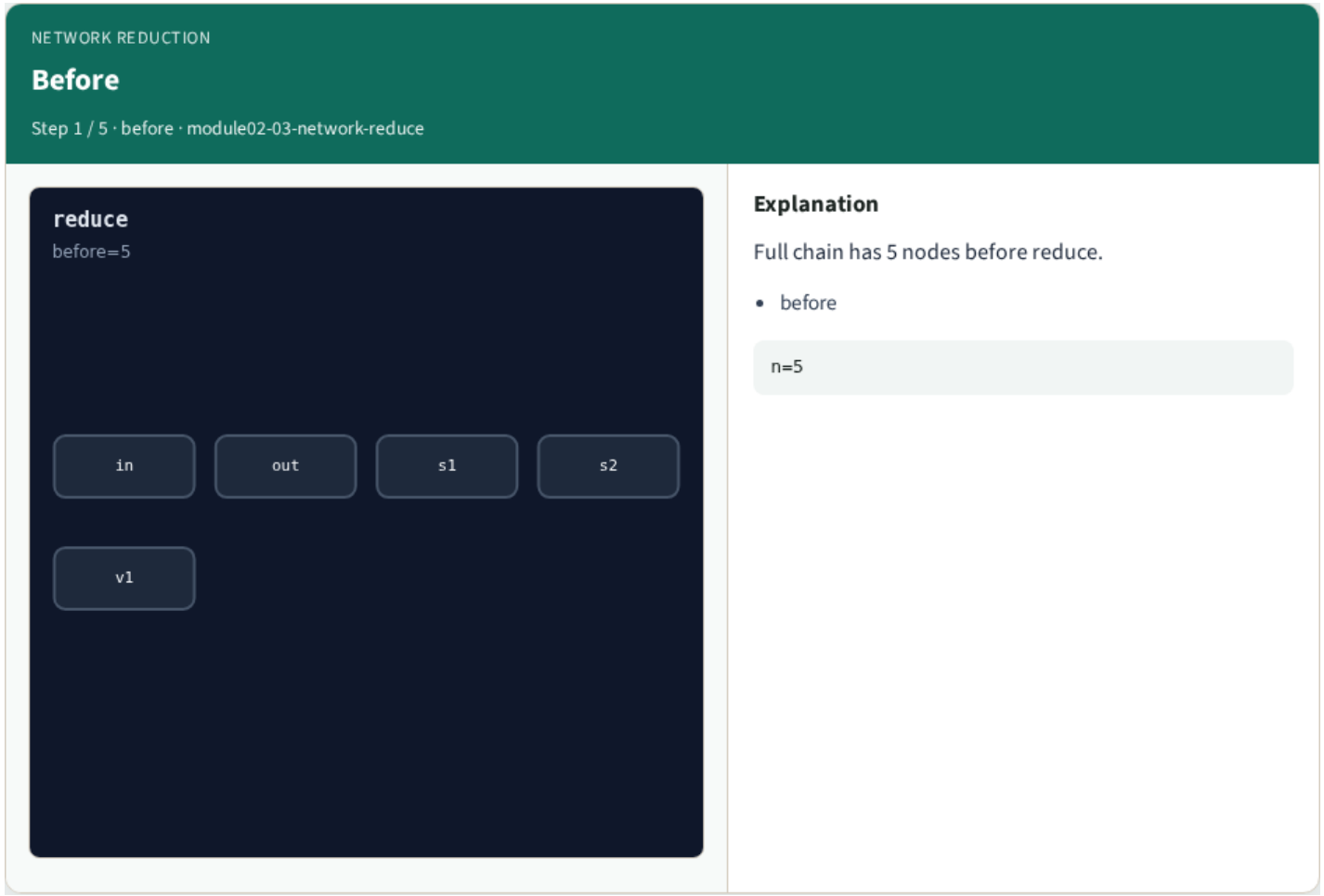


Before

Series R

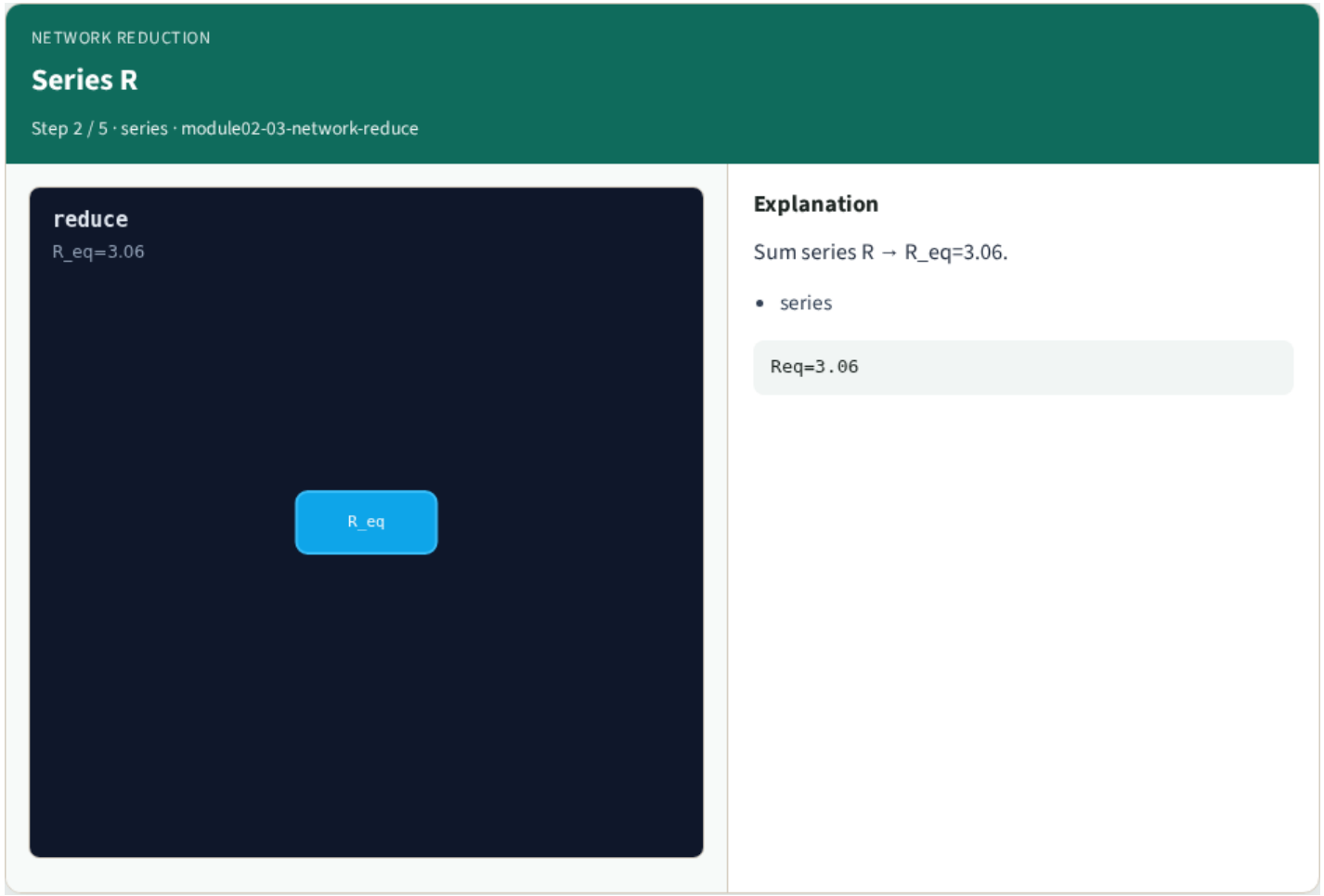


Series R

Sum C

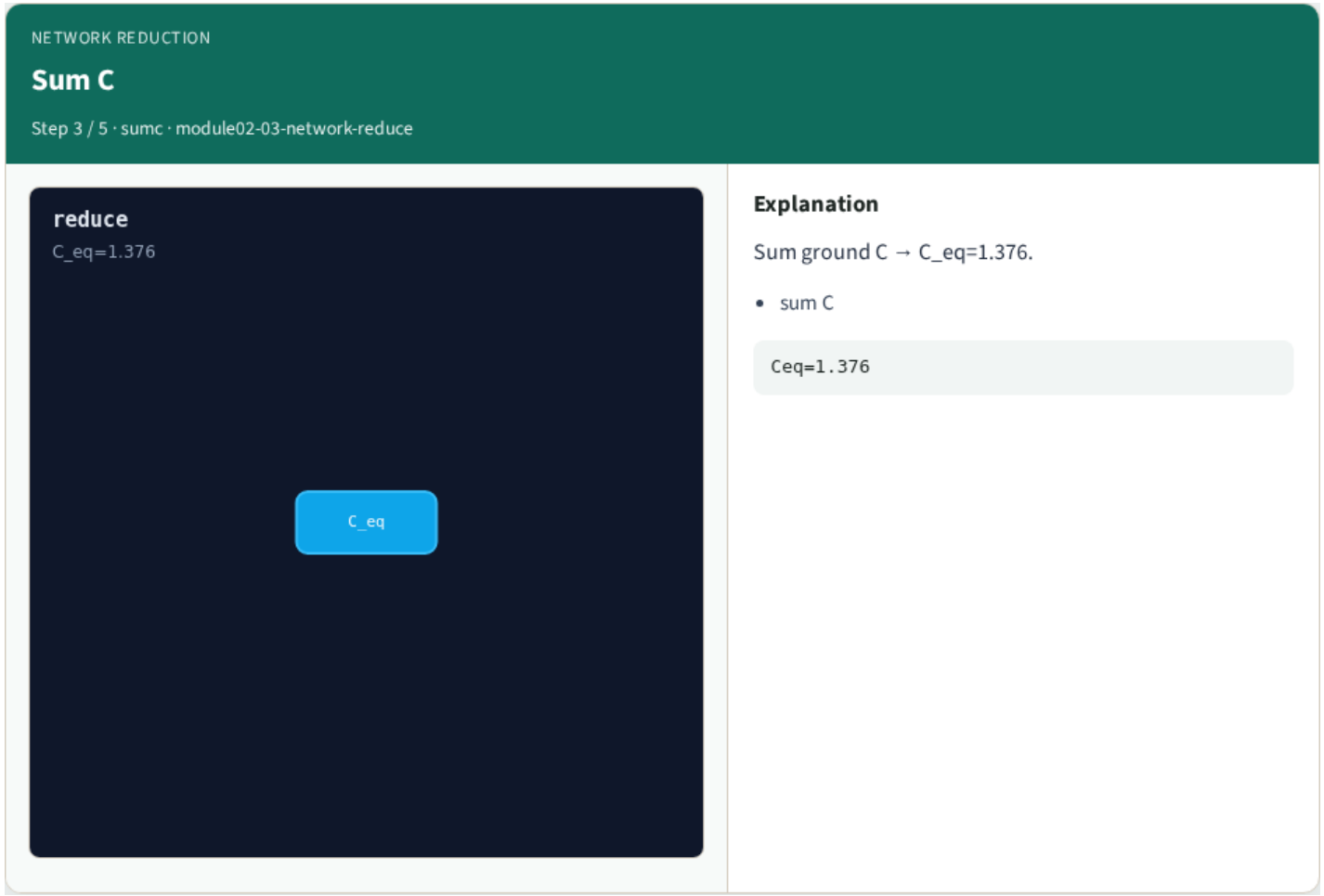
NETWORK REDUCTION
Sum C
Step 3 / 5 · sumc · module02-03-network-reduce
reduce
C_eq=1.376
C_eq
Explanation
Sum ground C → C_eq=1.376.
sum C
Ceq=1.376


Sum C

After

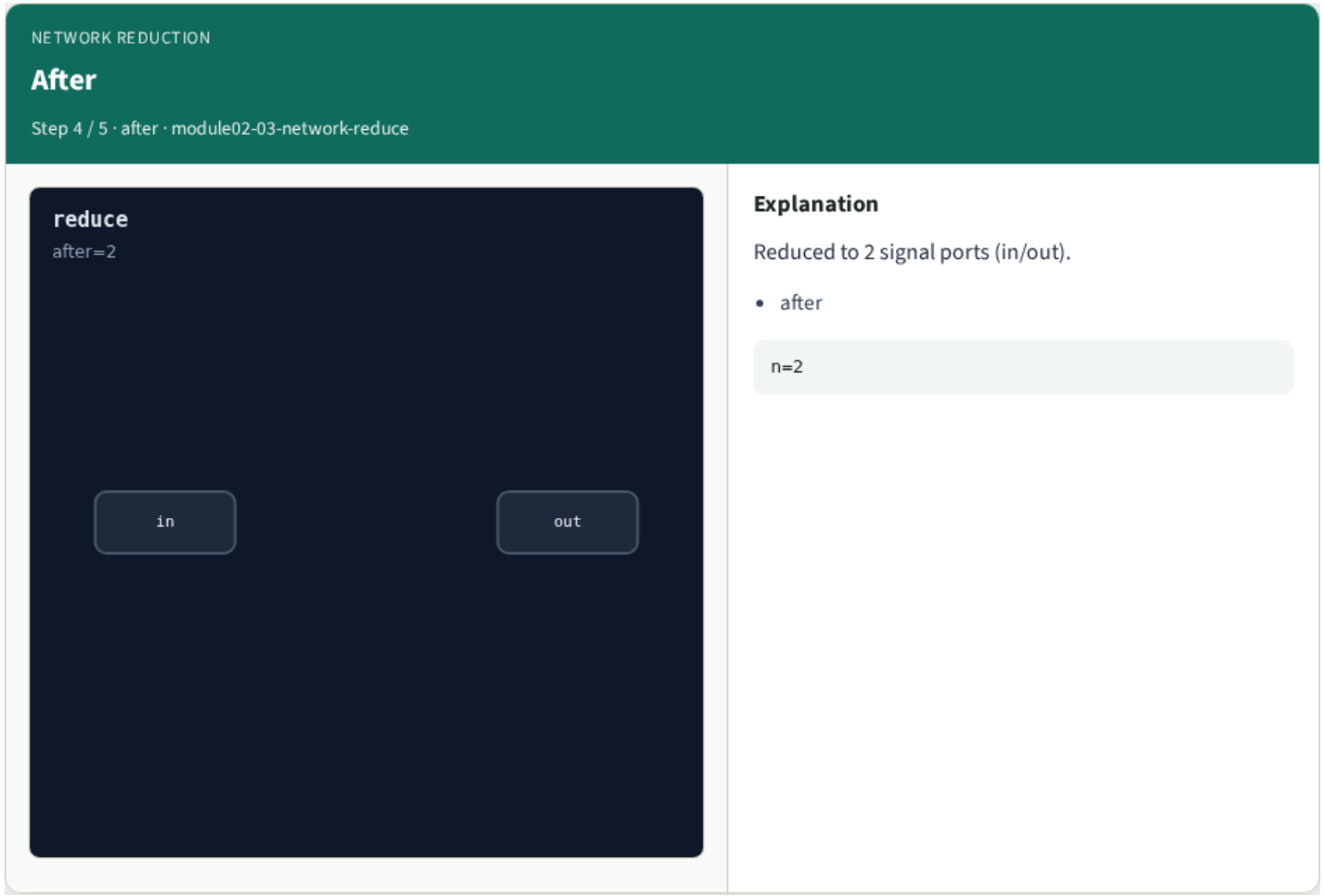
NETWORK REDUCTION
After
Step 4 / 5 · after · module02-03-network-reduce
reduce
after=2
in
out
Explanation
Reduced to 2 signal ports (in/out).
after
n=2


After

Golden

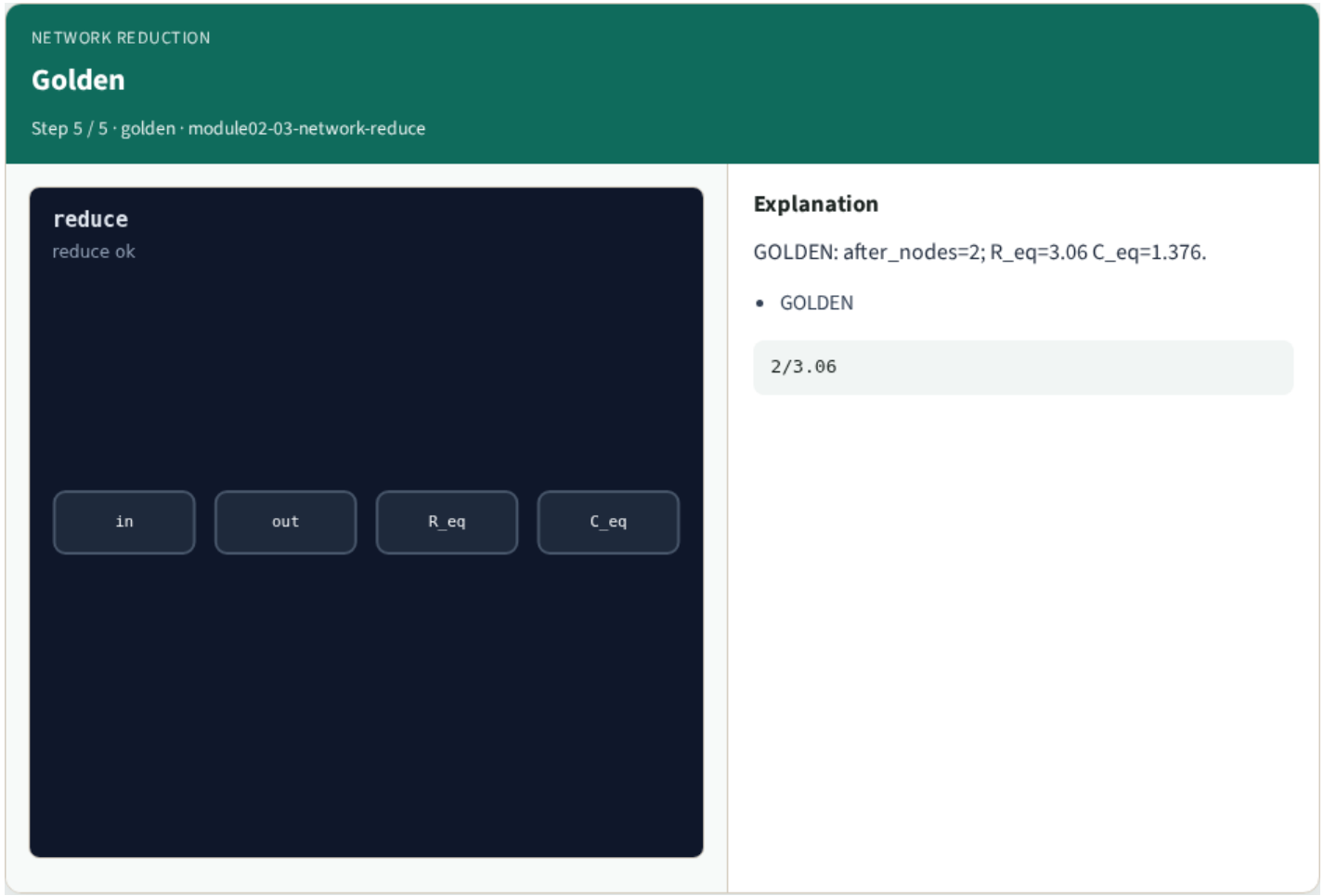

Golden

Browser lab track

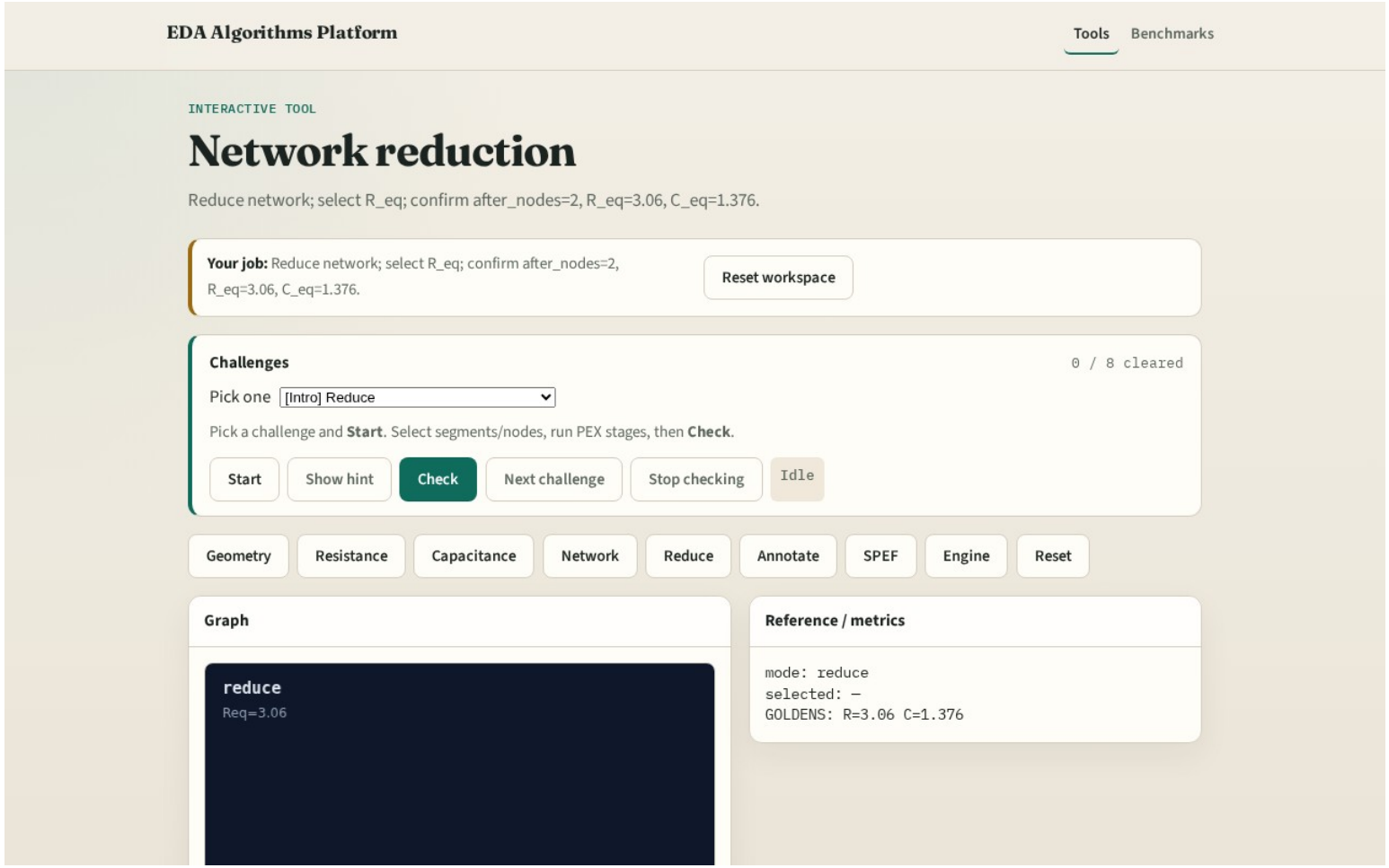

Browser lab starter

Implement track

- Call reduce_network(); assert after_nodes==2 and r_eq==3.06 and c_eq==1.376

Pitfalls

- Reducing C before R
- Keeping internal nodes after reduce

Your turn

- Next: back-annotate nets