Welcome

After PEX you need a circuit engine , MNA, Newton, LU, transient

The idea

- Toy tiny_spice: voltage divider V2=3; RC transient; diode 1-D Newton

Two tracks

- Implement track uses common/ solvers; browser lab track uses platform tools

Toy netlist

- Vin=5 V divider; R1=2, R2=3, Cload=1, Dprot , V2=3 DC; RC transient; diode Newton

Path

- Netlist → MNA → DC → sparse LU → Newton → callbacks → BE transient → engine

Begin

- Next: netlist nodes and ground